

Problem

Determine the complex power for the following cases:

(a) $P = 269 \text{ W}$, $Q = 150 \text{ VAR}$ (capacitive)

(b) $Q = 2000 \text{ VAR}$, $\text{pf} = 0.9$ (leading)

(c) $S = 600 \text{ VA}$, $Q = 450 \text{ VAR}$ (inductive)

(d) $V_{\text{rms}} = 220 \text{ V}$, $P = 1 \text{ kW}$,

$|Z| = 40 \Omega$ (inductive)

Step-by-step solution

Step 1 of 8

(a)

$$S = P - jQ$$

$$S = 269 - j150 \text{ VA}$$

Step 2 of 8

(b)

$$\text{Pf} = \cos \theta$$

$$0.9 = \cos \theta$$

$$\theta = 25.84^\circ$$

$$Q = 2000 \text{ VAR}$$

$$S = \frac{Q}{\sin \theta}$$

$$S = \frac{2000}{\sin(25.84^\circ)}$$

$$S = 4588.31$$

Step 3 of 8

$$P = S \cos \theta$$

$$P = 4588.31 \times \cos 25.84$$

$$P = 4129.48$$

Therefore,

$$S = P - jQ$$

$$S = 4129.48 - j2000 \text{ VA}$$

Step 4 of 8

(c)

$$S = 600 \text{ V A}$$

$$Q = 450 \text{ V AR}$$

$$S = \frac{Q}{\sin \theta}$$

$$\sin \theta = \frac{Q}{S}$$

$$\sin \theta = \frac{450}{600}$$

$$\sin \theta = 0.75$$

$$\theta = 48.59$$

Step 5 of 8

$$P = S \cos \theta$$

$$P = 600 \cos(48.59)$$

$$P = 396.86$$

Therefore,

$$S = 396.86 + j 450 \text{ VA}$$

Step 6 of 8

(d)

$$V_{\text{rms}} = 220\text{V},$$

$$P = 1\text{kW},$$

$$|Z| = 40\Omega$$

$$S = \frac{|V|^2}{|Z|}$$

$$S = \frac{(220)^2}{40}$$

$$S = 1210$$

Step 7 of 8

$$P = S \cos \theta$$

$$\cos \theta = \frac{P}{S}$$

$$\cos \theta = \frac{1000}{1210}$$

$$\cos \theta = 0.826$$

$$\theta = 34.31$$

Step 8 of 8

$$Q = S \sin \theta$$

$$Q = 1210 \sin(34.31)$$

$$Q = 682.041$$

Therefore,

$$\boxed{S = 1000 + j682.041 \text{ VA}}$$