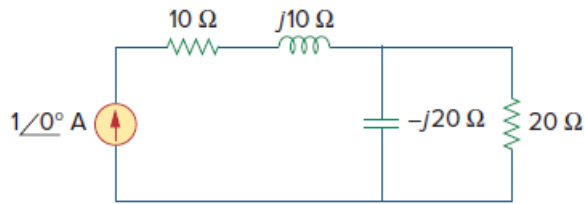


Problem

For the network in Fig. 11.73, find the complex power absorbed by each element.

Figure 11.73:



Step-by-step solution

Step 1 of 10

Refer to Figure 11.73 in the text book.

The current flowing through the $10\ \Omega$ resistor and $j10\ \Omega$ inductor is same as the value of the current source. That is, $1\angle 0^\circ\ \text{A}$.

The current $1\angle 0^\circ\ \text{A}$ divides between the $-j20\ \Omega$ capacitor and $20\ \Omega$ resistor.

Calculate the current I_{-j20} passing through the capacitor using current division rule.

$$\begin{aligned} I_{-j20} &= (1\angle 0^\circ) \left(\frac{20}{20 - j20} \right) \\ &= (1\angle 0^\circ) (0.5 + j0.5) \\ &= (1\angle 0^\circ) (0.707\angle 45^\circ) \\ &= 0.707\angle 45^\circ\ \text{A} \end{aligned}$$

Therefore, the value of the current I_{-j20} passing through the capacitor is $0.707\angle 45^\circ\ \text{A}$.

Step 2 of 10

Calculate the value of the current I_{20} passing through the $20\ \Omega$ resistor.

$$\begin{aligned} I_{20} &= (1\angle 0^\circ) \left(\frac{-j20}{20 - j20} \right) \\ &= (1\angle 0^\circ) (0.5 - j0.5) \\ &= (1\angle 0^\circ) (0.707\angle -45^\circ) \\ &= 0.707\angle -45^\circ\ \text{A} \end{aligned}$$

Therefore, the value of the current I_{20} passing through the resistor is $0.707\angle -45^\circ\ \text{A}$.

Step 3 of 10

Calculate the voltage across the $10\ \Omega$ resistor.

$$\begin{aligned} V_{10} &= (1\angle 0^\circ)(10) \\ &= 10\angle 0^\circ\ \text{V} \end{aligned}$$

Therefore, the voltage V_{10} across the $10\ \Omega$ resistor is $10\angle 0^\circ\ \text{V}$.

Step 4 of 10

Calculate the complex power S_{10} absorbed by the $10\ \Omega$ resistor.

$$S_{10} = \frac{1}{2} V_{10} I_{10}^*$$

Substitute $1\angle 0^\circ$ A for I_{10} and $10\angle 0^\circ$ V for V_{10} .

$$\begin{aligned} S_{10} &= \frac{1}{2} (10\angle 0^\circ) (1\angle 0^\circ)^* \\ &= (5\angle 0^\circ) (1\angle 0^\circ) \\ &= 5\angle 0^\circ \text{ VA} \end{aligned}$$

Therefore, the value of the complex power S_{10} is $5\angle 0^\circ \text{ VA}$.

Step 5 of 10

Calculate the voltage across the $j10\ \Omega$ inductor.

$$\begin{aligned} V_{j10} &= (1\angle 0^\circ) (j10) \\ &= (1\angle 0^\circ) (10\angle 90^\circ) \\ &= 10\angle 90^\circ \text{ V} \end{aligned}$$

Therefore, the voltage V_{j10} across the $j10\ \Omega$ resistor is $10\angle 90^\circ$ V.

Step 6 of 10

Calculate the complex power S_{j10} absorbed by the $j10\ \Omega$ inductor.

$$S_{j10} = \frac{1}{2} V_{j10} I_{j10}^*$$

Substitute $1\angle 0^\circ$ A for I_{j10} and $10\angle 90^\circ$ V for V_{j10} .

$$\begin{aligned} S_{j10} &= \frac{1}{2} (10\angle 90^\circ) (1\angle 0^\circ)^* \\ &= (5\angle 90^\circ) (1\angle 0^\circ) \\ &= 5\angle 90^\circ \text{ VA} \end{aligned}$$

Therefore, the value of the complex power S_{j10} is $5\angle 90^\circ \text{ VA}$.

Step 7 of 10

Calculate the voltage across the $20\ \Omega$ resistor.

$$V_{20} = I_{20} (20)$$

Substitute $0.707\angle -45^\circ$ A for I_{20} .

$$\begin{aligned} V_{20} &= (0.707\angle -45^\circ) (20) \\ &= 14.14\angle -45^\circ \text{ V} \end{aligned}$$

Therefore, the voltage V_{20} across the $20\ \Omega$ resistor is $14.14\angle -45^\circ$ V.

Step 8 of 10

Calculate the complex power S_{20} absorbed by the $20\ \Omega$ resistor.

$$S_{20} = \frac{1}{2} V_{20} I_{20}^*$$

Substitute $0.707\angle -45^\circ$ for I_{20} and $14.14\angle -45^\circ$ V for V_{20} .

$$\begin{aligned} S_{20} &= \frac{1}{2} (14.14\angle -45^\circ)(0.707\angle -45^\circ)^* \\ &= (7.07\angle -45^\circ)(0.707\angle 45^\circ) \\ &= 5\angle 0^\circ \text{ VA} \end{aligned}$$

Therefore, the value of the complex power S_{20} is $5\angle 0^\circ \text{ VA}$.

Step 9 of 10

Calculate the voltage across the $-j20\ \Omega$ capacitor.

$$V_{-j20} = I_{-j20}(-j20)$$

Substitute $0.707\angle 45^\circ$ A for I_{-j20} .

$$\begin{aligned} V_{-j20} &= (0.707\angle 45^\circ)(20\angle -90^\circ) \\ &= 14.14\angle -45^\circ \text{ V} \end{aligned}$$

Therefore, the voltage V_{-j20} across the $-j20\ \Omega$ capacitor is $14.14\angle -45^\circ$ V.

Step 10 of 10

Calculate the complex power S_{-j20} absorbed by the $-j20\ \Omega$ capacitor.

$$S_{-j20} = \frac{1}{2} V_{-j20} I_{-j20}^*$$

Substitute $0.707\angle 45^\circ$ for I_{-j20} and $14.14\angle -45^\circ$ V for V_{-j20} .

$$\begin{aligned} S_{-j20} &= \frac{1}{2} (14.14\angle -45^\circ)(0.707\angle 45^\circ)^* \\ &= (7.07\angle -45^\circ)(0.707\angle -45^\circ) \\ &= 5\angle -90^\circ \text{ VA} \end{aligned}$$

Therefore, the value of the complex power S_{-j20} is $5\angle -90^\circ \text{ VA}$.