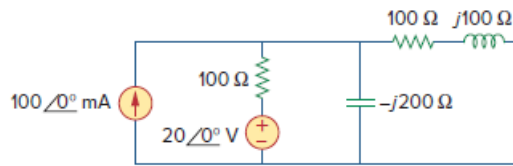


Problem

Calculate the reactive power in the inductor and capacitor in the circuit of Fig. 11.78.

Figure 11.78:



Step-by-step solution

Step 1 of 9

Refer to Figure 11.78 in the text book.

Consider the circuit diagram shown in Figure 1.

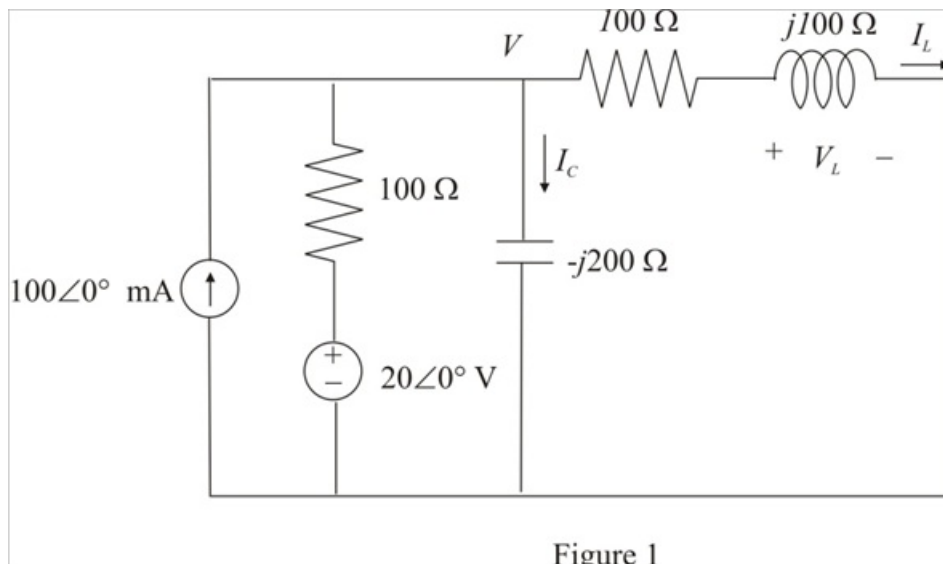


Figure 1

Step 2 of 9

Hand calculations:

Apply Kirchhoff's Current Law at node-1.

$$-100\angle 0^\circ \text{ m} + \frac{V - 20\angle 0^\circ}{100} + \frac{V}{-j200} + \frac{V}{100 + j100} = 0 \dots\dots (1)$$

$$-100\angle 0^\circ \text{ m} + \frac{V}{100} - \frac{20\angle 0^\circ}{100} + \frac{V}{-j200} + \frac{V}{100 + j100} = 0$$

$$V \left(\frac{1}{100} + \frac{1}{-j200} + \frac{1}{100 + j100} \right) = 0.1\angle 0^\circ + 0.2\angle 0^\circ$$

$$V (0.01 + j0.005 + 0.005 - j0.005) = 0.3\angle 0^\circ$$

$$V (0.015\angle 0^\circ) = 0.3\angle 0^\circ$$

$$V = \frac{0.3\angle 0^\circ}{0.015\angle 0^\circ}$$

$$V = 20\angle 0^\circ \text{ V}$$

Therefore, the value of the voltage V is $20\angle 0^\circ \text{ V}$.

Step 3 of 9

Calculate the value of the current through the inductor.

$$I_L = \frac{V}{100 + j100} \dots\dots (2)$$

Substitute $20\angle 0^\circ$ V for V .

$$\begin{aligned} I_L &= \frac{20\angle 0^\circ}{100 + j100} \\ &= \frac{20\angle 0^\circ}{141.42\angle 45^\circ} \\ &= 0.141\angle -45^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current passing through the inductor is $0.141\angle -45^\circ$ A.

Step 4 of 9

Calculate the value of the voltage across the inductor.

$$V_L = (100 + j100)I_L \dots\dots (3)$$

Substitute $0.141\angle -45^\circ$ A for I_L .

$$\begin{aligned} V_L &= (141.42\angle 45^\circ)(0.141\angle -45^\circ) \\ &= (141.42\angle 45^\circ)(0.141\angle -45^\circ) \\ &= 19.94 \text{ V} \end{aligned}$$

Therefore, the value of the voltage across the inductor is 19.94 V.

Step 5 of 9

Calculate the value of the reactive power in the inductor.

$$Q_L = \text{Im}(V_L I_L^*) \dots\dots (4)$$

Substitute 19.94 V for V_L and $0.141\angle -45^\circ$ A for I_L .

$$\begin{aligned} Q_L &= \text{Im}(19.94 \times (0.141\angle -45^\circ)^*) \\ &= \text{Im}(19.94 \times 0.141\angle 45^\circ) \\ &= \text{Im}(2.81\angle 45^\circ) \\ &= \text{Im}(2 + j2) \end{aligned}$$

$$Q_L = 2 \text{ VAR}$$

Therefore, the value of the reactive power in the inductor is 2 VAR .

Step 6 of 9

Calculate the value of the current through the capacitor.

$$I_c = \frac{V}{-j200} \dots\dots (5)$$

Substitute $20\angle 0^\circ$ V for V .

$$\begin{aligned} I_c &= \frac{20\angle 0^\circ}{-j200} \\ &= \frac{20\angle 0^\circ}{200\angle -90^\circ} \\ &= 0.1\angle 90^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current passing through the capacitor is $0.1\angle 90^\circ$ A .

Step 7 of 9

Calculate the value of the reactive power in the capacitor.

$$Q_c = \text{Im}(VI_c^*) \dots\dots (6)$$

Substitute $20\angle 0^\circ$ V for V_L and $0.1\angle 90^\circ$ A for I_L .

$$\begin{aligned} Q_c &= \text{Im}(20\angle 0^\circ \times (0.1\angle 90^\circ)^*) \\ &= \text{Im}(20 \times 0.1\angle -90^\circ) \\ &= \text{Im}(2\angle -90^\circ) \\ &= \text{Im}(0 - j2) \end{aligned}$$

$$Q_c = -2 \text{ VAR}$$

Therefore, the value of the reactive power in the capacitor is -2 VAR .

Step 8 of 9

MATLAB calculations:

Use equations (1), (2), (3), (4), (5) and (6) in MATLAB to solve the problem.

Write the following instructions in MATLAB m-file and save the program.

```
syms V
```

```
V = solve(-0.1+((V-20)/100)+(V/-200i)+(V/(100+100i)))%NODAL EQUATION%
```

```
IL = V/(100+100i)%INDUCTOR CURRENT%
```

```
VL = IL*(100+100i)%INDUCTOR VOLTAGE%
```

```
QL = imag(VL*conj(IL))%INDUCTOR REACTIVE POWER%
```

```
IC = (V/-200i)%CAPCITOR CURRENT%
```

```
QC = imag(v*conj(IC))%CAPACITOR REACTIVE POWER%
```

Step 9 of 9

Run the program and view the results in the command window.

$$V = 20$$

$$I_L = 1/10 - i/10$$

$$V_L = 20$$

$$Q_L = 2$$

$$I_C = i/10$$

$$Q_C = -2$$

Therefore, the values of the reactive power in the inductor and the capacitor are 2 VAR

and -2 VAR respectively.