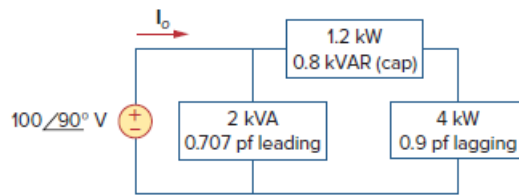


Problem

Given the circuit in Fig. 11.80, find I_o and the overall complex power supplied.

Figure 11.80:



Step-by-step solution

Step 1 of 7

Refer to Figure 11.80 in the text book.

Draw the following block diagram.

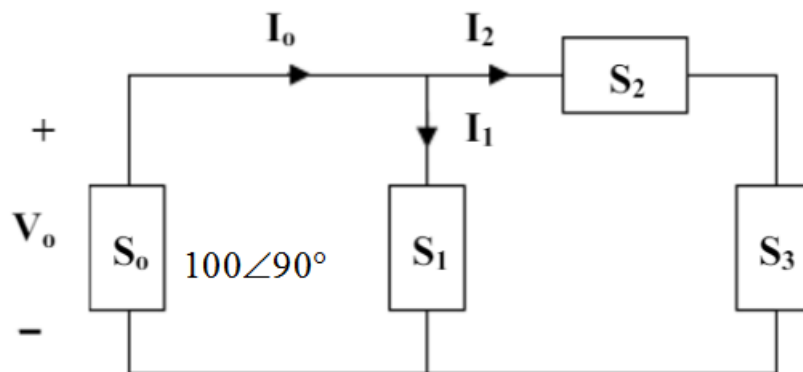


Figure 1

Step 2 of 7

Write the expression of complex power S_1 .

$$\begin{aligned}
 S_1 &= P - jQ \\
 &= P - j\left(\frac{P}{\cos\theta}\right)\sin(\cos^{-1}(\theta)) \\
 &= 2 \times 10^3 \times 0.707 - j\left(\frac{1414}{0.707}\right)\sin(\cos^{-1}(0.707)) \\
 &= 1414 - j1414.43 \text{ VA}
 \end{aligned}$$

Since power factor is leading, the reactive power is negative.

Write the expression of complex power S_2 .

$$\begin{aligned}
 S_2 &= P - jQ \\
 &= 1.2 - j0.8 \text{ kVA}
 \end{aligned}$$

Since power factor is leading, the reactive power is negative.

Step 3 of 7

Write the expression of complex power S_3 .

$$\begin{aligned} S_3 &= P + jQ \\ &= P + j \left(\frac{P}{\cos \theta} \right) \sin(\cos^{-1}(\theta)) \\ &= 4 + j \left(\frac{4 \text{ kW}}{0.9} \right) \sin(\cos^{-1}(0.9)) \\ &= 4 + j1.937 \text{ kVA} \end{aligned}$$

Since power factor is lagging, the reactive power is positive.

The loads S_2 and S_3 are in series. Consider S_4 as equivalent load.

$$\begin{aligned} S_4 &= S_2 + S_3 \\ &= 1.2 - j0.8 \text{ kVA} + 4 + j1.937 \text{ kVA} \\ &= 5.2 + j1.137 \text{ kVA} \end{aligned}$$

Step 4 of 7

Determine the value of current I_2 .

$$\begin{aligned} S_4 &= V_o I_2^* \\ I_2^* &= \frac{S_4}{V_o} \\ &= \frac{5.2 + j1.137 \text{ kVA}}{100 \angle 90^\circ} \\ &= \frac{5323 \angle 12.34^\circ}{100 \angle 90^\circ} \\ &= 53.23 \angle -77.66^\circ \text{ A} \end{aligned}$$

Hence,

$$I_2 = 53.23 \angle 77.66^\circ \text{ A}$$

Step 5 of 7

Determine the value of current I_1 .

$$\begin{aligned} S_1 &= V_o I_1^* \\ I_1^* &= \frac{S_1}{V_o} \\ &= \frac{1414 - j1414.43}{100 \angle 90^\circ} \\ &= \frac{2000 \angle -45^\circ}{100 \angle 90^\circ} \\ &= 20 \angle -135^\circ \text{ A} \end{aligned}$$

Hence,

$$I_1 = 20 \angle 135^\circ \text{ A}$$

Step 6 of 7

Determine the value of $\mathbf{I}_o$ using Kirchhoff's current law.

$$\begin{aligned}\mathbf{I}_o &= \mathbf{I}_1 + \mathbf{I}_2 \\ &= 20\angle 135^\circ + 53.23\angle 77.66^\circ \\ &= 66.2\angle 92.4^\circ \text{ A}\end{aligned}$$

Therefore, the value of current $\mathbf{I}_o$ is $66.2\angle 92.4^\circ \text{ A}$.

Step 7 of 7

Determine the overall complex power supplied.

$$\begin{aligned}\mathbf{S}_o &= \mathbf{V}_o \mathbf{I}_o^* \\ &= (100\angle 90^\circ)(66.2\angle 92.4^\circ)^* \\ &= 6.62\angle -2.4^\circ \text{ kVA}\end{aligned}$$

Therefore, the overall complex power supplied is $6.62\angle -2.4^\circ \text{ kVA}$.