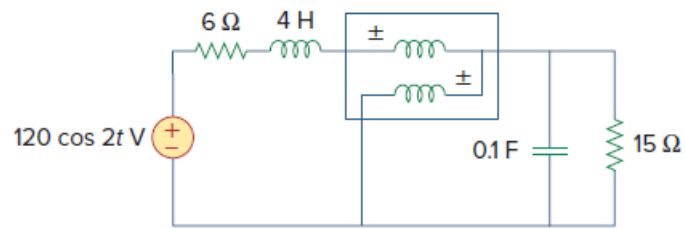


Problem

What is the reading of the wattmeter in the network of Fig. 11.92?

Figure 11.92:



Step-by-step solution

Step 1 of 4

The wattmeter measures the power absorbed by the parallel combination of 0.1 F & 150 Ω.

$$120 \cos(2t) \Rightarrow 120 \angle 0^\circ$$

$$\omega = 2 \text{ rad/sec}$$

$$4 \text{ H} = j\omega L$$

$$4 \text{ H} = j8 \Omega$$

$$0.1 \text{ F} = \frac{1}{j\omega C}$$

$$0.1 \text{ F} = -j5 \Omega$$


$$Z = 15 \Omega \parallel (-j5 \Omega)$$

$$Z = \frac{15(-j5)}{15 - j5}$$

$$Z = 1.5 - j4.5 \Omega$$

Step 2 of 4

Consider the following circuit,

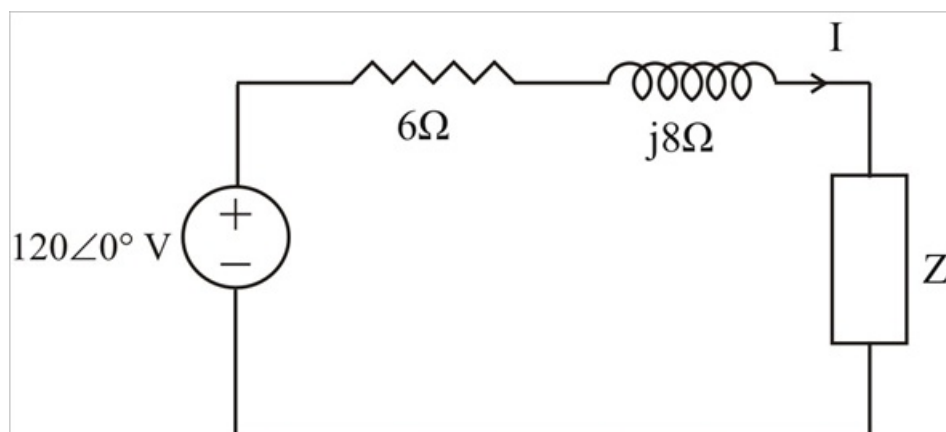

Step 3 of 4

$$I = \frac{120}{(6 + j8) + (1.5 - j4.5)}$$

$$I = \frac{120}{7.5 + j3.5}$$

$$I = 14.5 \angle -25.02^\circ \text{ A}$$

Step 4 of 4

$$S = \frac{1}{2} V \times I^*$$

$$S = \frac{1}{2} |I|^2 \times Z$$

$$S = \frac{1}{2} \times (14.5)^2 \times (1.5 - j4.5)$$

$$S = 157.69 - j473.06$$

The wattmeter reads,

$$P = \text{Re}(S) = \boxed{157.69 \text{ W}}$$