

Problem

The nameplate of an electric motor has the following information:

Line voltage: 220 V rms

Line current: 15 A rms

Line frequency: 60 Hz

Power: 2700 W

Determine the power factor (lagging) of the motor. Find the value of the capacitance C that must be connected across the motor to raise the pf to unity.

Step-by-step solution

Step 1 of 1

$$P = S \cos \theta$$

$$P f = \cos \theta = \frac{P}{S} = \frac{2700}{(220)(15)} = 0.8182$$

$$Q = S \sin \theta = 220(15) \sin(35.09^\circ) = 1897.3$$

When the power is raised to unity $P f$, Q_{120° .

$$\text{And, } Q_c = Q = 1897.3$$

$$C = \frac{Q_L}{\omega V_{rms}^2} = \frac{1897.3}{(2\pi)(60)(220)^2}$$

$$= 104 \mu F$$