


Problem

A coupling capacitor is used to block dc current from an amplifier as shown in Fig. 11.98(a). The amplifier and the capacitor act as the source, while the speaker is the load as in Fig. 11.98(b).

(a) At what frequency is maximum power transferred to the speaker?

(b) If $V_s = 4.6 \text{ V rms}$, how much power is delivered to the speaker at that frequency?

Figure 11.98:

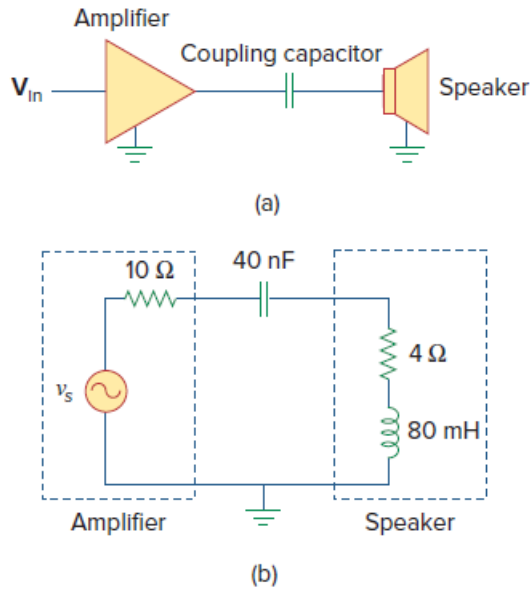

Step-by-step solution

Step 1 of 2

$$(A) \text{ Source impedance } Z_S = R_S - jX_C$$

$$\text{Load impedance } Z_L = R_L + jX_L$$

For maximum load transfer,

$$Z_L = Z_S^* \Rightarrow R_S = R_L, \quad X_C = X_L$$

$$X_C = X_L \Rightarrow \frac{1}{\omega C} = \omega L$$

$$\text{Or, } \omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(80 \times 10^{-3})(40 \times 10^{-9})}}$$

$$= 2.814 \text{ KHz}$$

Step 2 of 2

$$(B) P = \left(\frac{V_s}{10+4} \right)^2 4 = \left(\frac{4.6}{14} \right)^2 4$$

$$= 431.8 \text{ mW} \quad [\text{Since } V_s \text{ in RMS}]$$