

Problem

Given that $\mathbf{V}_{bn} = 220\angle 30^\circ \text{ V}$ find $\mathbf{V}_{an}$ and $\mathbf{V}_{cn}$, assuming a positive (*abc*) sequence.

Step-by-step solution

Step 1 of 3

Refer to Figure 12.7 in the textbook.

Consider the value of $\mathbf{V}_{bn}$.

$$\mathbf{V}_{bn} = 220\angle 30^\circ \text{ V}$$

Compare with $V_p\angle\theta^\circ$.

Therefore, the value of V_p is 220 V and θ° is 30° .

Step 2 of 3

Notice that $\mathbf{V}_{an}$ leads $\mathbf{V}_{bn}$ by 120° .

Calculate the value of $\mathbf{V}_{an}$.

$$\mathbf{V}_{an} = V_p\angle(\theta^\circ + 120^\circ)$$

Substitute 220 V for V_p and 30° for θ° .

$$\begin{aligned}\mathbf{V}_{an} &= 220\angle(30^\circ + 120^\circ) \\ &= 220\angle 150^\circ \text{ V}\end{aligned}$$

Hence, the value of the phase voltage $\mathbf{V}_{an}$ is $220\angle 150^\circ \text{ V}$.

Step 3 of 3

Notice that $\mathbf{V}_{bn}$ leads $\mathbf{V}_{cn}$ by 120° .

Calculate the value of $\mathbf{V}_{cn}$.

$$\mathbf{V}_{cn} = V_p\angle(\theta^\circ - 120^\circ)$$

Substitute 220 V for V_p and 30° for θ° .

$$\begin{aligned}\mathbf{V}_{cn} &= 220\angle(30^\circ - 120^\circ) \\ &= 220\angle -90^\circ \text{ V}\end{aligned}$$

Hence, the value of the phase voltage $\mathbf{V}_{cn}$ is $220\angle -90^\circ \text{ V}$.