

Problem

What is the phase sequence of a three-phase motor for which $\mathbf{V}_{AN} = 220\angle -100^\circ \text{ V}$

and $\mathbf{V}_{BN} = 220\angle 140^\circ \text{ V}$?

(a) *abc*

(b) *acb*

Step-by-step solution

Step 1 of 3

Refer to Figure 12.7 for the phase sequences in the textbook.

The phase sequence of a three-phase motor is,

$$\mathbf{V}_{AN} = 220\angle -100^\circ \text{ V}$$

$$\mathbf{V}_{BN} = 220\angle 140^\circ \text{ V}$$

$$= 220\angle (-100^\circ + 240^\circ) \text{ V}$$

Therefore,

$$\mathbf{V}_{CN} = 220\angle (-100^\circ + 120^\circ) \text{ V}$$

Step 2 of 3

For the *acb* or negative sequence, the phase equations are,

$$\mathbf{V}_{AN} = 220\angle -100^\circ \text{ V}$$

$$\mathbf{V}_{BN} = 220\angle (-100^\circ + 120^\circ) \text{ V}$$

$$= 220\angle 20^\circ \text{ V}$$

And,

$$\mathbf{V}_{CN} = 220\angle (-100^\circ - 120^\circ) \text{ V}$$

$$= 220\angle (-220^\circ) \text{ V}$$

Therefore, option (b) is not the answer.

Step 3 of 3

For the *abc* or positive sequence, the phase equations are,

$$\mathbf{V}_{AN} = 220\angle -100^\circ \text{ V}$$

$$\mathbf{V}_{BN} = 220\angle 140^\circ \text{ V}$$

$$= 220\angle (-100^\circ - 120^\circ) \text{ V}$$

$$= 220\angle (-100^\circ + 240^\circ) \text{ V}$$

Therefore,

$$\mathbf{V}_{CN} = 220\angle (-100^\circ + 120^\circ) \text{ V}$$

Therefore, the correct answer is option **(a)**.