

Chapter 12, Problem 3P

Problem

Given a balanced Y-connected three-phase generator with a line-to-line voltage of

$V_{ab} = 100\angle 45^\circ \text{ V}$ and $V_{bc} = 100\angle 165^\circ \text{ V}$, determine the phase sequence and the value of V_{ca} .

Step-by-step solution

Step 1 of 2

Consider the given values.

$$V_{ab} = 100\angle 45^\circ \text{ V and } V_{bc} = 100\angle 165^\circ \text{ V}.$$

The voltages are in negative or *acb* sequence since the voltage V_{bc} leads V_{ab} by 120° .

Compare $V_{ab} = 100\angle 45^\circ \text{ V}$ with $V_L\angle \theta^\circ$.

The values of V_L and θ° are 100 V and 45° respectively.

Step 2 of 2

Calculate the value of the voltage V_{ca} .

$$\begin{aligned} V_{ca} &= V_L\angle \theta^\circ - 120^\circ \\ &= 100\angle 45^\circ - 120^\circ \\ &= 100\angle -75^\circ \text{ V} \end{aligned}$$

Substitute 45° for θ° and 100 V for V_L .

$$\begin{aligned} V_{ca} &= 100\angle 45^\circ - 120^\circ \\ &= 100\angle -75^\circ \text{ V} \end{aligned}$$

Therefore, the phase voltage V_{ca} is, $100\angle -75^\circ \text{ V}$.