

Problem

Which of these is not a required condition for a balanced system:

- (a) $|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$
- (b) $\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$
- (c) $\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$
- (d) Source voltages are 120° out of phase with each other.
- (e) Load impedances for the three phases are equal.

Step-by-step solution**Step 1** of 1

(C)