

Chapter 12, Problem 4P

Problem

A three-phase system with abc sequence and $V_L = 440$ V feeds a Y-connected load with

$$Z_L = 40\angle 30^\circ \Omega . \text{ Find the line currents.}$$

Step-by-step solution

Step 1 of 2

The line voltage is, $V_L = 440$ V

Calculate the phase voltage.

$$\begin{aligned} V_p &= \frac{V_L}{\sqrt{3}} \\ &= \frac{440}{\sqrt{3}} \\ &= 254 \text{ V} \end{aligned}$$

The phase sequence is abc .

Therefore,

$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ &= 254 \angle 0^\circ \text{ V} \\ V_{bn} &= V_p \angle -120^\circ \\ &= 254 \angle -120^\circ \text{ V} \\ V_{cn} &= V_p \angle 120^\circ \\ &= 254 \angle 120^\circ \text{ V} \end{aligned}$$

Step 2 of 2

Calculate the line currents.

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_L}$$

Substitute $254\angle 0^\circ$ V for $\mathbf{V}_{an}$ and $40\angle 30^\circ$ for $\mathbf{Z}_L$.

$$\begin{aligned}\mathbf{I}_a &= \frac{254\angle 0^\circ}{40\angle 30^\circ} \\ &= 6.35\angle -30^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_b &= \frac{\mathbf{V}_{bn}}{\mathbf{Z}_L} \\ &= \frac{254\angle -120^\circ}{40\angle 30^\circ} \\ &= 6.35\angle -150^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_c &= \frac{\mathbf{V}_{cn}}{\mathbf{Z}_L} \\ &= \frac{254\angle 120^\circ}{40\angle 30^\circ} \\ &= 6.35\angle 90^\circ \text{ A}\end{aligned}$$

Therefore, the line currents are,

$\mathbf{I}_a = 6.35\angle -30^\circ \text{ A}$
$\mathbf{I}_b = 6.35\angle -150^\circ \text{ A}$
$\mathbf{I}_c = 6.35\angle 90^\circ \text{ A}$