

Chapter 12, Problem 4RQ

Problem

In a Y-connected load, the line current and phase current are equal.

- (a) True
- (b) False

Step-by-step solution

Step 1 of 1

(A)