

Chapter 12, Problem 5RQ

Problem

In a Δ -connected load, the line current and phase current are equal.

- (a) True
- (b) False

Step-by-step solution

Step 1 of 1

(B)