

Chapter 12, Problem 6RQ

Problem

In a Y-Y system, a line voltage of 220 V produces a phase voltage of:

- (a) 381 V
- (b) 311 V
- (c) 220 V
- (d) 156 V
- (e) 127 V

Step-by-step solution

Step 1 of 1

(C)