

## Chapter 12, Problem 7RQ

### Problem

In a  $\Delta$ - $\Delta$  system, a phase voltage of 100 V produces a line voltage of:

- (a) 58 V
- (b) 71 V
- (c) 100 V
- (d) 173 V
- (e) 141 V

### Step-by-step solution

#### Step 1 of 1

( C )