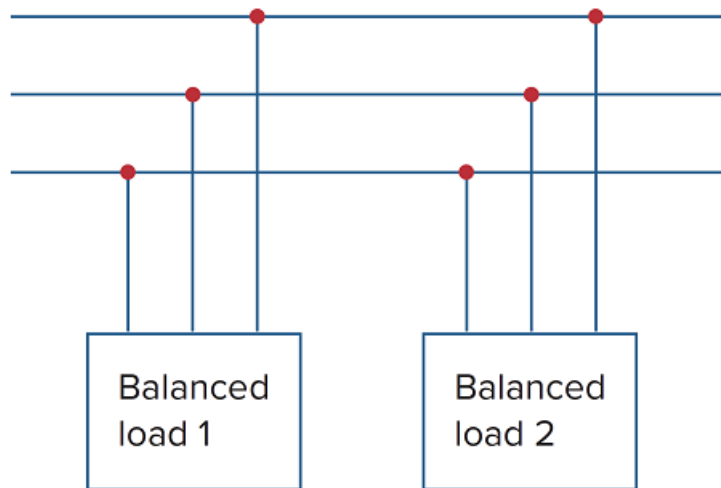



Problem

Assume that the two balanced loads in Fig. 12.22(a) are supplied by an 840-V rms 60-Hz line. Load 1 is Y-connected with $30 + j40 \, \Omega$ per phase, while load 2 is a balanced three-phase motor drawing 48 kW at a power factor of 0.8 lagging. Assuming the abc sequence, calculate: (a) the complex power absorbed by the combined load, (b) the kVAR rating of each of the three capacitors Δ -connected in parallel with the load to raise the power factor to unity, and (c) the current drawn from the supply at unity power factor condition.

Figure 12.22



(a)

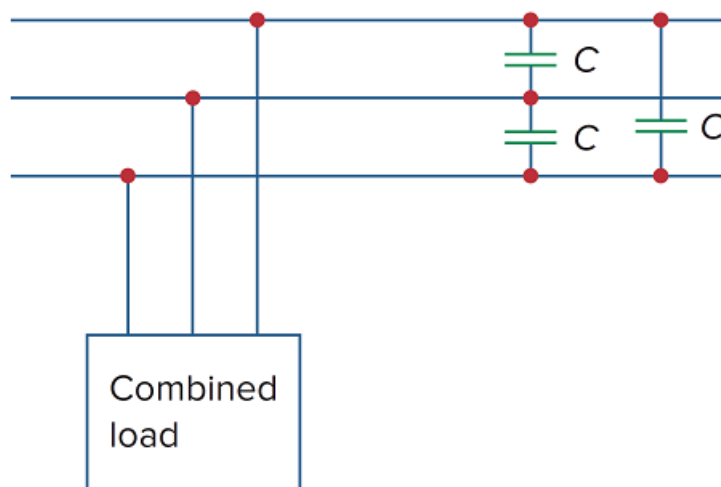


(b)

Step-by-step solution

Step 1 of 5

Given figures are

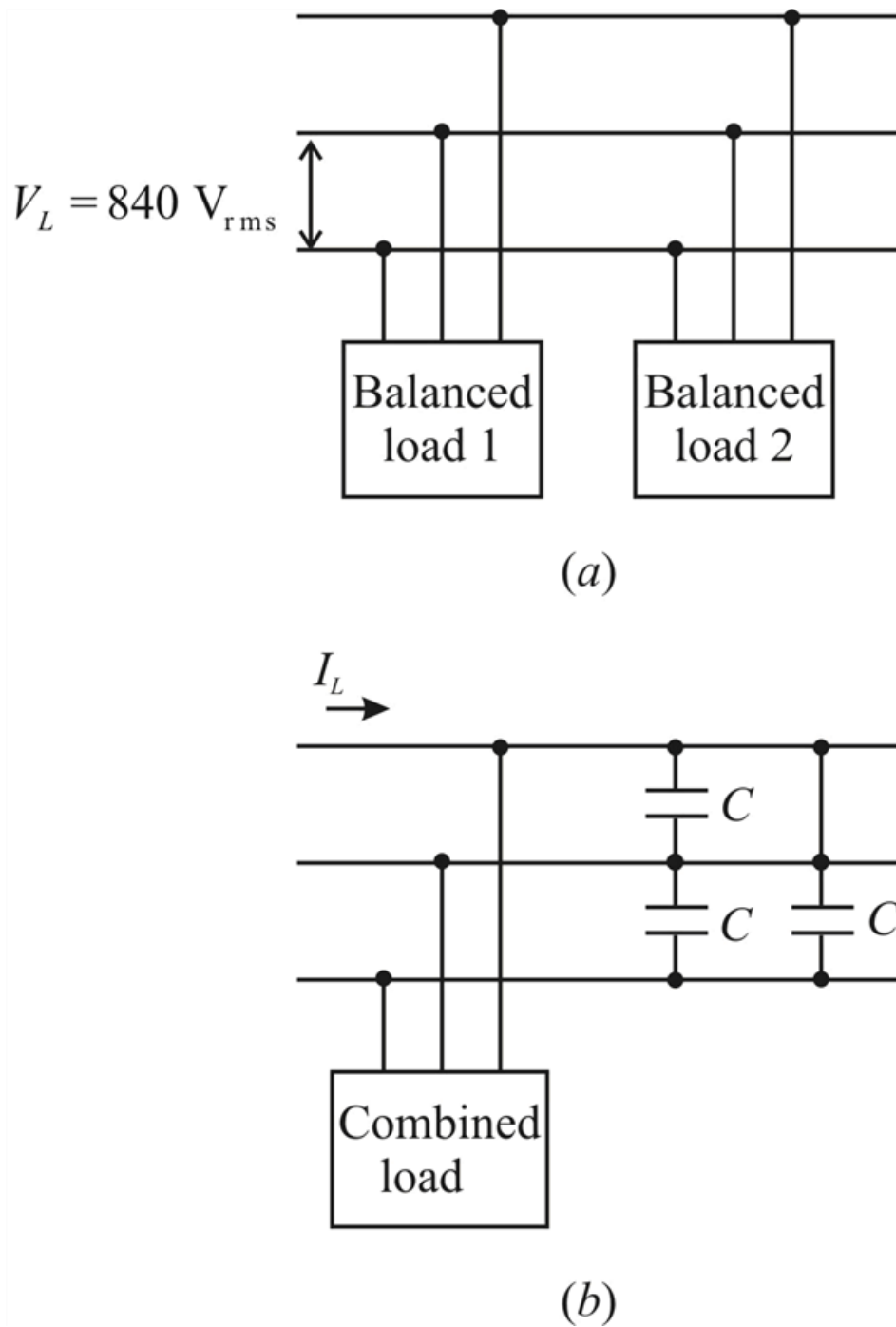

Step 2 of 5

For load

$$Z = 30 + j40\Omega$$

We have

$$S_1 = \frac{V_{\text{rms}}^2}{Z^*}$$

$$S_1 = \frac{(840)^2}{30 - j40}$$

$$\therefore S_1 = 8.4672 + j11.29 \text{ kVA}$$

Step 3 of 5

For load 2,

$$P_2 = 48 \text{ kW}$$

$$\cos \theta_2 = 0.8$$

$$\therefore \theta_2 = 36.87^\circ$$

Hence

$$Q_2 = S_2 \sin \theta_2$$

$$Q_2 = \left(\frac{P_2}{\cos \theta_2} \right) \sin (36.87^\circ)$$

$$Q_2 = \left(\frac{48 \times 10^3}{0.8} \right) \times 0.6$$

$$Q_2 = 36 \text{ kVAR}$$

$$\therefore S_2 = P_2 + jQ_2$$

$$S_2 = 48 + j36 \text{ kVA}$$

Step 4 of 5

(a) Therefore the complex power absorbed by the combined load is

$$S = S_1 + S_2$$

$$S = ((8.4672 + j11.29) + (48 + j36)) \text{ kVA}$$

$$\therefore \boxed{S = 56.47 + j47.29 \text{ kVA}}$$

(or)

$$\boxed{S = 73.656 \angle 39.84^\circ \text{ kVA}}$$

The real power (P) = 56.47 kW

The reactive power (Q) = 47.29 kVAR

Power factor (pf) = $\cos(39.94^\circ)$

$$pf = 0.7667$$

Step 5 of 5

(b)

New power factor in unity

$$\cos \theta_{new} = 1$$

$$\theta_{new} = 0^\circ$$

We have

$$Q_c = P(\tan \theta_{old} - \tan \theta_{new})$$

$$Q_c = (56.47 \times 10^3)(\tan(39.94^\circ) - \tan(0^\circ))$$

$$\therefore Q_c = 47.28 \text{ kVAR}$$

For each capacitor the rating is $\frac{47.258 \times 10^3}{3}$

$$= \boxed{15.76 \text{ kVR}}$$

(c) Given that

$$pf = \cos \theta = 1$$

Since $S = \frac{P}{\cos \theta}$

$$S = \frac{56.47 \times 10^3}{1}$$

$$S = 56.47 \text{ kVA}$$

Therefore

$$I_L = \frac{S}{\sqrt{3} \times V_L}$$

$$I_L = \frac{56.47 \times 10^3}{\sqrt{3} \times 840}$$

$$\therefore \boxed{I_L = 38.813 \text{ A}}$$