

Chapter 12, Problem 8RQ

Problem

When a Y-connected load is supplied by voltages in abc phase sequence, the line voltages lag the corresponding phase voltages by 30° .

- (a) True
- (b) False

Step-by-step solution

Step 1 of 1

(B)