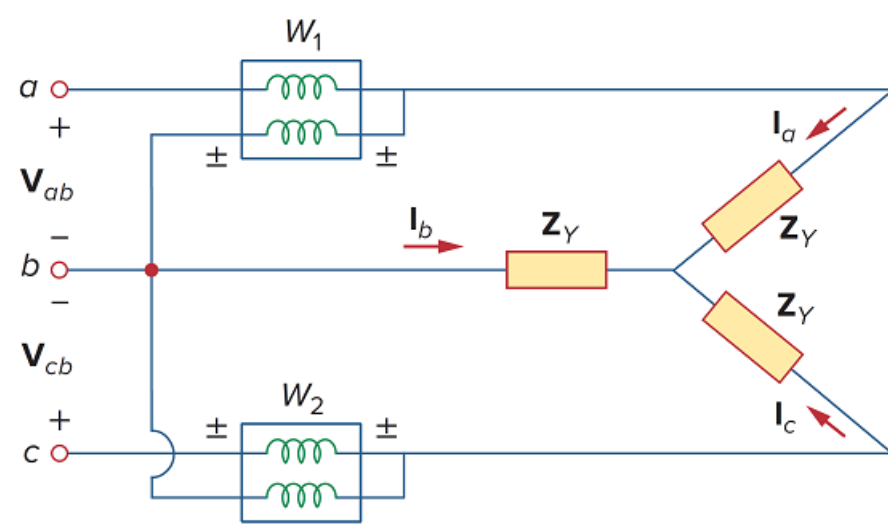


Problem

If the load in Fig. 12.35 is delta-connected with impedance per phase of $Z_p = 30 + j40 \Omega$ and $V_L = 220 \text{ V}$, predict the readings of the wattmeters W_1 and W_2 . Calculate PT and QT .

Figure 12.35



Step-by-step solution

Step 1 of 6

Convert the delta connected load to wye connection.

Calculate the impedance of the wye connected load.

$$Z_Y = \frac{Z_\Delta}{3}$$

Substitute $30 + j40 \Omega$ for Z_Δ .

$$\begin{aligned} Z_Y &= \frac{30 + j40}{3} \\ &= \frac{50 \angle 53.13^\circ}{3} \\ &= 16.667 \angle 53.13^\circ \Omega \end{aligned}$$

Therefore, the impedance of the wye connected load is, $16.667 \angle 53.13^\circ \Omega$.

The magnitude of the load $|Z_Y|$ is 16.667Ω and the phase angle θ° is 53.13° .

Step 2 of 6

Refer to Figure 12.35 in the text book.

Calculate the magnitude value of the line current I_L .

$$I_L = \frac{V_L}{\sqrt{3}|Z_Y|}$$

Substitute $16.667 \angle 53.13^\circ \Omega$ for $|Z_Y|$ and 220 V for V_L .

$$\begin{aligned} I_L &= \frac{220}{\sqrt{3}(16.667)} \\ &= \frac{220}{28.868} \\ &= 7.621 \text{ A} \end{aligned}$$

Therefore, the magnitude value of the line current I_L is 7.621 A .

Step 3 of 6

Calculate the value of the power reading in wattmeter W_1 .

$$W_1 = V_L I_L \cos(\theta^\circ + 30^\circ)$$

Substitute 220 V for V_L , 7.621 A for I_L and 53.13° for θ° .

$$\begin{aligned} W_1 &= (220)(7.621)\cos(53.13^\circ + 30^\circ) \\ &= (1676.62)\cos(83.13^\circ) \\ &= (1676.62)(0.1196) \\ &= 200.52 \text{ W} \end{aligned}$$

Therefore, the value of the power reading in wattmeter W_1 is 200.52 W .

Step 4 of 6

Calculate the value of the power reading in wattmeter W_2 .

$$W_2 = V_L I_L \cos(\theta^\circ - 30^\circ)$$

Substitute 220 V for V_L , 7.621 A for I_L and 53.13° for θ° .

$$\begin{aligned} W_2 &= (220)(7.621)\cos(53.13^\circ - 30^\circ) \\ &= (1676.62)\cos(23.13^\circ) \\ &= (1676.62)(0.9196) \\ &= 1.5418 \text{ kW} \end{aligned}$$

Therefore, the value of the power reading in wattmeter W_2 is 1.5418 kW .

Step 5 of 6

Calculate the value of the total real power P_T absorbed by the load.

$$P_T = W_1 + W_2$$

Substitute 1.5418 kW for W_2 and 200.52 W for W_1 .

$$\begin{aligned} P_T &= 200.52 + 1.5418 \text{ k} \\ &= 1.7423 \text{ kW} \end{aligned}$$

Therefore, the value of the total real power P_T absorbed by the load is 1.7423 kW .

Step 6 of 6

Calculate the value of the total reactive power Q_r absorbed by the load.

$$Q_r = \sqrt{3}(W_2 - W_1)$$

Substitute 1.5418 kW for W_2 and 200.52 W for W_1 .

$$\begin{aligned} Q_r &= \sqrt{3}(1.5418 \text{ k} - 200.52) \\ &= \sqrt{3}(1.3413 \text{ k}) \\ &= 2.3232 \text{ kVAR} \end{aligned}$$

Therefore, the value of the total reactive power Q_r absorbed by the load is 2.3232 kVAR.