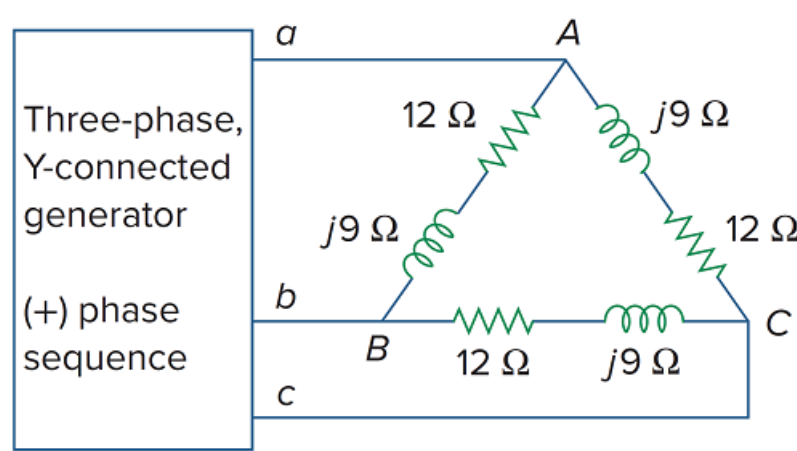


Problem

If $\mathbf{V}_{an} = 220 \angle 60^\circ \text{ V}$ in the network of Fig. 12.49, find the load phase currents $\mathbf{I}_{AB}$, $\mathbf{I}_{BC}$, and $\mathbf{I}_{CA}$.

Figure 12.49



Step-by-step solution

Step 1 of 5

Draw the following circuit diagram:

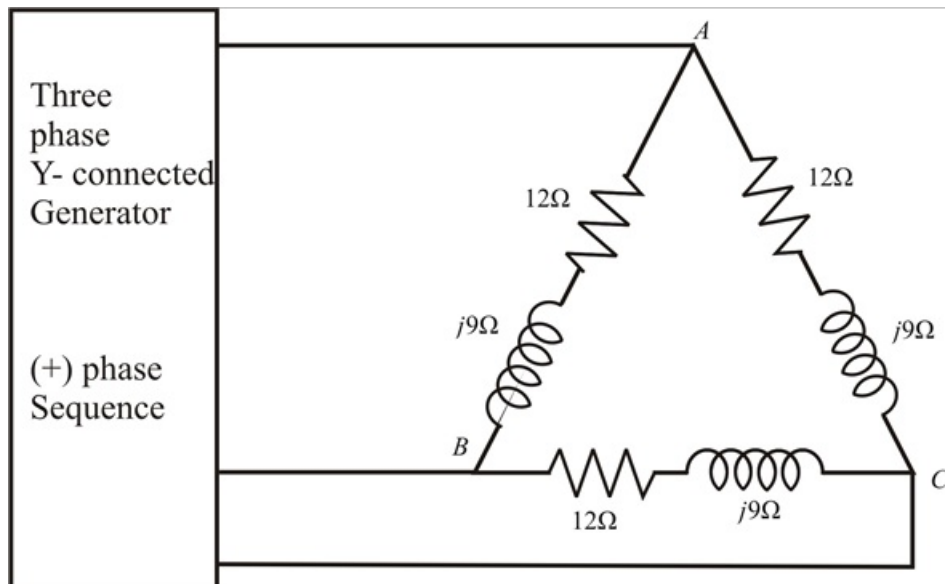


Figure 1

Step 2 of 5

Consider the voltage $V_{an} = 220\angle 60^\circ \text{ V}$.

Write the expression for the line voltage V_{AB} .

$$\begin{aligned} V_{AB} &= \sqrt{3}V_{an}\angle 30^\circ \\ &= \sqrt{3} \times 220\angle (60^\circ + 30^\circ) \\ &= 381.05\angle 90^\circ \text{ V} \end{aligned}$$

Therefore, the value of line voltage V_{AB} is $381.05\angle 90^\circ \text{ V}$.

Step 3 of 5

Calculate the value of the phase current I_{AB} .

Write the expression for phase currents I_{AB} .

$$\begin{aligned} I_{AB} &= \frac{V_{AB}}{Z_{AB}} \\ &= \frac{381.05\angle 90^\circ}{12 + j9} \\ &= \frac{381.05\angle 90^\circ}{15\angle 36.86^\circ} \\ &= 25.40\angle 53.13^\circ \text{ A} \end{aligned}$$

Therefore, the value of line currents I_{AB} is $25.40\angle 53.13^\circ \text{ A}$.

Step 4 of 5

Calculate the value of the phase current I_{BC} .

Write the expression for phase currents I_{BC} for a balanced system.

$$\begin{aligned} I_{BC} &= I_{AB}\angle -120^\circ \\ &= 25.40\angle (53.13^\circ - 120^\circ) \\ &= 25.40\angle -66.87^\circ \text{ A} \end{aligned}$$

Therefore, the value of phase current I_{BC} is $25.40\angle -66.87^\circ \text{ A}$.

Step 5 of 5

Calculate the value of the phase current I_{CA} .

Write the expression for phase currents I_{CA} for a balanced system.

$$\begin{aligned} I_{CA} &= I_{AB}\angle 120^\circ \\ &= 25.40\angle (53.13^\circ + 120^\circ) \\ &= 25.40\angle 173.13^\circ \text{ A} \end{aligned}$$

Therefore, the value of phase current I_{CA} is $25.40\angle 173.13^\circ \text{ A}$.