

Problem

A balanced delta connected source is connected to a balanced delta connected load where $Z_L = (80 + j60) \Omega$ and $Z_l = (2 + j) \Omega$. Given that the load voltages are

$$\mathbf{V}_{AB} = 100 \angle 0^\circ \text{ V}, \mathbf{V}_{BC} = 100 \angle 120^\circ \text{ V}, \text{ and}$$

$$\mathbf{V}_{CA} = 100 \angle -120^\circ \text{ V. Calculate the source voltages } \mathbf{V}_{ab}, \mathbf{V}_{bc}, \text{ and } \mathbf{V}_{ca}.$$

Step-by-step solution

Step 1 of 10

Consider the circuit diagram shown in Figure 1.

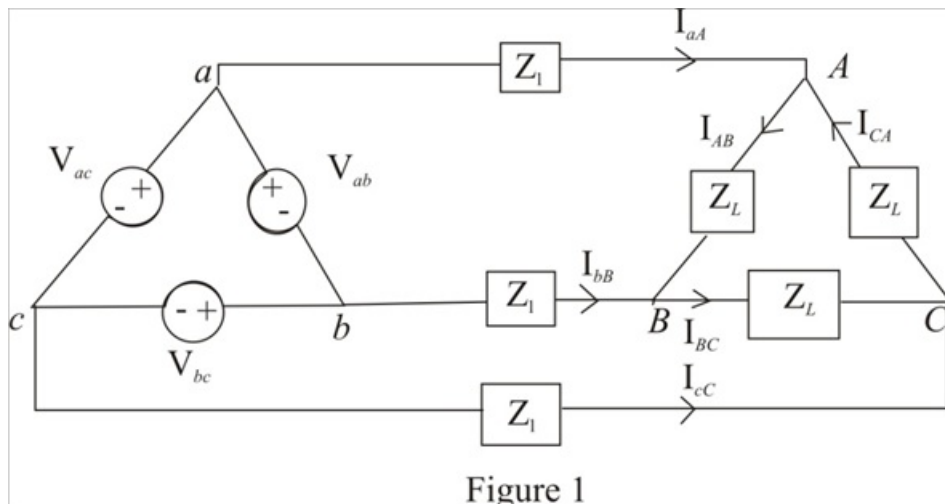


Figure 1

Step 2 of 10

Calculate the value of the current $\mathbf{I}_{AB}$.

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_L}$$

Substitute $100 \angle 0^\circ \text{ V}$ for $\mathbf{V}_{AB}$ and $80 + j60 \Omega$ for $\mathbf{Z}_L$.

$$\begin{aligned} \mathbf{I}_{AB} &= \frac{100 \angle 0^\circ}{80 + j60} \\ &= \frac{100 \angle 0^\circ}{100 \angle 36.87^\circ} \\ &= 1 \angle -36.87^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current $\mathbf{I}_{AB}$ is, $1 \angle -36.87^\circ \text{ A}$.

Step 3 of 10

Calculate the value of the current I_{BC} .

$$I_{BC} = \frac{V_{BC}}{Z_L}$$

Substitute $100\angle 120^\circ$ V for V_{BC} and $80 + j60 \Omega$ for Z_L .

$$\begin{aligned} I_{BC} &= \frac{100\angle 120^\circ}{80 + j60} \\ &= \frac{100\angle 120^\circ}{100\angle 36.87^\circ} \\ &= 1\angle 83.13^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_{BC} is, $1\angle 83.13^\circ$ A.

Step 4 of 10

Calculate the value of the current I_{AC} .

$$I_{AC} = \frac{V_{AC}}{Z_L}$$

Substitute $100\angle -120^\circ$ V for V_{AC} and $80 + j60 \Omega$ for Z_L .

$$\begin{aligned} I_{AC} &= \frac{100\angle -120^\circ}{80 + j60} \\ &= \frac{100\angle -120^\circ}{100\angle 36.87^\circ} \\ &= 1\angle -156.87^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_{AC} is, $1\angle -156.87^\circ$ A.

Step 5 of 10

Calculate the value of the line current I_{aA} .

$$I_{aA} = I_{AB} - I_{AC}$$

Substitute $1\angle -36.87^\circ$ A for I_{AB} and $1\angle -156.87^\circ$ A for I_{AC} .

$$\begin{aligned} I_{aA} &= 1\angle -36.87^\circ - 1\angle -156.87^\circ \\ &= 1.732\angle -6.87^\circ \text{ A} \end{aligned}$$

Therefore, the value of the line current I_{aA} is, $1.732\angle -6.87^\circ$ A.

Step 6 of 10

Calculate the value of the line current I_{bB} .

$$I_{bB} = I_{BC} - I_{AB}$$

Substitute $1\angle -36.87^\circ$ A for I_{AB} and $1\angle 83.13^\circ$ A for I_{BC} .

$$\begin{aligned} I_{bB} &= 1\angle 83.13^\circ - 1\angle -36.87^\circ \\ &= 1.732\angle 113.13^\circ \text{ A} \end{aligned}$$

Therefore, the value of the line current I_{bB} is, $1.732\angle 113.13^\circ$ A.

Step 7 of 10

Calculate the value of the line current I_{cC} .

$$I_{cC} = I_{CA} - I_{BC}$$

Substitute $1\angle -156.87^\circ$ A for I_{CA} and $1\angle 83.13^\circ$ A for I_{BC} .

$$\begin{aligned} I_{cC} &= 1\angle -156.87^\circ - 1\angle 83.13^\circ \\ &= 1.732\angle -126.87^\circ \text{ A} \end{aligned}$$

Therefore, the value of the line current I_{cC} is, $1.732\angle -126.87^\circ$ A.

Step 8 of 10

Calculate the value of the source voltage V_{ab} .

$$\begin{aligned} V_{ab} &= I_{aA}Z_L + V_{AB} - I_{bB}Z_L \\ &= (I_{aA} - I_{bB})Z_L + V_{AB} \end{aligned}$$

Substitute $1.732\angle -6.87^\circ$ A for I_{aA} , $1.732\angle 113.13^\circ$ A for I_{bB} , $100\angle 0^\circ$ V for V_{AB} and $2 + j1 \Omega$ for Z_L .

$$\begin{aligned} V_{ab} &= (1.732\angle -6.87^\circ - 1.732\angle 113.13^\circ)(2 + j1) + 100\angle 0^\circ \\ &= (3\angle -36.87^\circ)(2.236\angle 26.57^\circ) + 100\angle 0^\circ \\ &= 6.708\angle -10.3^\circ + 100\angle 0^\circ \\ &= 106.61\angle -0.65^\circ \text{ V} \end{aligned}$$

Therefore, the value of the line voltage V_{ab} is $106.61\angle -0.65^\circ$ V.

Step 9 of 10

Calculate the value of the source voltage V_{bc} .

$$\begin{aligned} V_{bc} &= I_{bB}Z_L + V_{BC} - I_{cC}Z_L \\ &= (I_{bB} - I_{cC})Z_L + V_{BC} \end{aligned}$$

Substitute $1.732\angle -126.87^\circ$ A for I_{cC} , $1.732\angle 113.13^\circ$ A for I_{bB} , $100\angle 120^\circ$ V for V_{BC} and $2 + j1 \Omega$ for Z_L .

$$\begin{aligned} V_{bc} &= (1.732\angle 113.13^\circ - 1.732\angle -126.87^\circ)(2 + j1) + 100\angle 120^\circ \\ &= (3\angle 83.13^\circ)(2.236\angle 26.57^\circ) + 100\angle 120^\circ \\ &= 6.708\angle 10.97^\circ + 100\angle 120^\circ \\ &= 106.61\angle 119.36^\circ \text{ V} \end{aligned}$$

Therefore, the value of the line voltage V_{bc} is $106.61\angle 119.36^\circ$ V.

Step 10 of 10

Calculate the value of the source voltage V_{ca} .

$$\begin{aligned} V_{ca} &= I_{cC}Z_L + V_{CA} - I_{aA}Z_L \\ &= (I_{cC} - I_{aA})Z_L + V_{CA} \end{aligned}$$

Substitute $1.732\angle -126.87^\circ$ A for I_{cC} , $1.732\angle -6.87^\circ$ A for I_{aA} , $100\angle -120^\circ$ V for V_{CA} and $2 + j1 \Omega$ for Z_L .

$$\begin{aligned} V_{ca} &= (1.732\angle -126.87^\circ - 1.732\angle -6.87^\circ)(2 + j1) + 100\angle -120^\circ \\ &= (3\angle -156.87^\circ)(2.236\angle 26.57^\circ) + 100\angle -120^\circ \\ &= 6.708\angle -130.3^\circ + 100\angle -120^\circ \\ &= 106.61\angle -120.65^\circ \text{ V} \end{aligned}$$

Therefore, the value of the line voltage V_{ca} is $106.61\angle -120.65^\circ \text{ V}$.