

Problem

The line-to-line voltages in a Y-load have a magnitude of 880 V and are in the positive sequence at 60 Hz. If the loads are balanced with $Z_1 = Z_2 = Z_3 = 25\angle 30^\circ$, find all line currents and phase voltages.

Step-by-step solution

Step 1 of 6

Refer to Figure 12.8 in the text book.

Calculate the value of the line current I_a .

$$I_a = \frac{V_{AB} \angle -30^\circ}{\sqrt{3}Z_Y}$$

Substitute $880\angle 0^\circ$ V for V_{AB} and $25\angle 30^\circ \Omega$ for Z_Y .

$$\begin{aligned} I_a &= \frac{880 \angle -30^\circ}{\sqrt{3}(25 \angle 30^\circ)} \\ &= \frac{880 \angle -30^\circ}{43.30 \angle 30^\circ} \\ &= 20.32 \angle -60^\circ \text{ A} \end{aligned}$$

Therefore, the value of the line current I_a is $20.32 \angle -60^\circ \text{ A}$.

Step 2 of 6

Calculate the value of the current I_b .

$$I_b = I_a \angle -120^\circ$$

Substitute $20.32 \angle -60^\circ \text{ A}$ for I_a .

$$\begin{aligned} I_b &= (20.32 \angle -60^\circ)(1 \angle -120^\circ) \\ &= 20.32 \angle -180^\circ \text{ A} \end{aligned}$$

Therefore, the value of the line current I_b is $20.32 \angle -180^\circ \text{ A}$.

Step 3 of 6

Calculate the value of the current I_c .

$$I_c = I_a \angle 120^\circ$$

Substitute $20.32 \angle -60^\circ \text{ A}$ for I_a .

$$\begin{aligned} I_c &= (20.32 \angle -60^\circ)(1 \angle 120^\circ) \\ &= 20.32 \angle 60^\circ \text{ A} \end{aligned}$$

Therefore, the value of the line current I_c is $20.32 \angle 60^\circ \text{ A}$.

Step 4 of 6

Calculate the value of the phase voltage V_{an} .

$$V_{an} = \frac{V_{AB} \angle -30^\circ}{\sqrt{3}}$$

Substitute $880 \angle 0^\circ$ V for V_{AB} .

$$\begin{aligned} V_{an} &= \frac{880 \angle -30^\circ}{\sqrt{3}} \\ &= 508.07 \angle -30^\circ \text{ V} \end{aligned}$$

Therefore, the value of the phase voltage V_{an} is $508.07 \angle -30^\circ$ V.

Step 5 of 6

Calculate the value of the voltage V_{bn} .

$$V_{bn} = V_{an} \angle -120^\circ$$

Substitute $508.07 \angle -30^\circ$ V for V_{an} .

$$\begin{aligned} V_{bn} &= (508.07 \angle -30^\circ)(1 \angle -120^\circ) \\ &= 508.07 \angle -150^\circ \text{ V} \end{aligned}$$

Therefore, the value of the phase voltage V_{bn} is $508.07 \angle -150^\circ$ V.

Step 6 of 6

Calculate the value of the voltage V_{cn} .

$$V_{cn} = V_{an} \angle 120^\circ$$

Substitute $508.07 \angle -30^\circ$ V for V_{an} .

$$\begin{aligned} V_{cn} &= (508.07 \angle -30^\circ)(1 \angle 120^\circ) \\ &= 508.07 \angle 90^\circ \text{ V} \end{aligned}$$

Therefore, the value of the phase voltage V_{cn} is $508.07 \angle 90^\circ$ V.