

Problem

A balanced three-phase Y- Δ system has $\mathbf{V}_{an} = 240\angle 0^\circ$ V rms and $\mathbf{Z}_\Delta = 51 + j45\ \Omega$. If the line impedance per phase is $0.4 + j1.2\ \Omega$, find the total complex power delivered to the load.

Step-by-step solution

Step 1 of 4

Consider the following balanced $Y-\Delta$ connection:

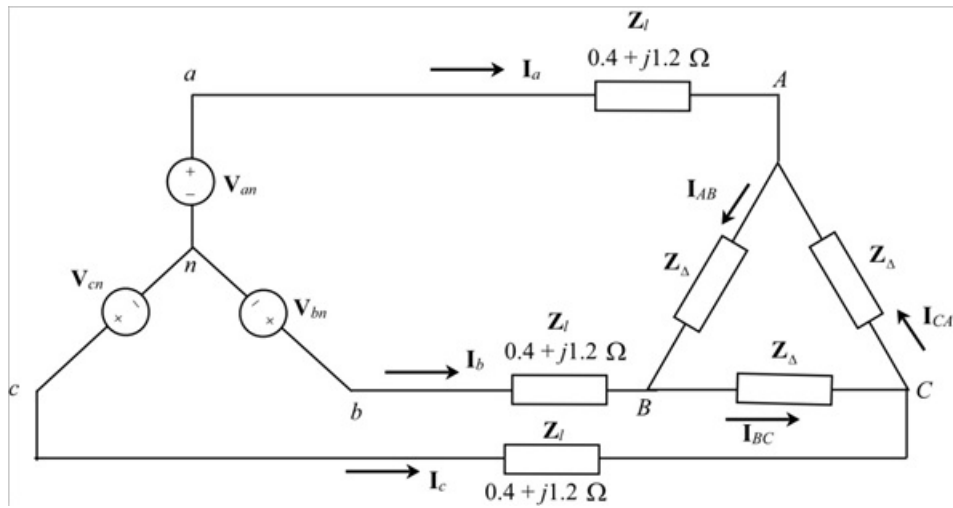


Figure 1

The load is delta connected. Convert delta load into equivalent Y-connected load.

The load impedance is,

$$Z_{\Delta} = 51 + j45 \, \Omega$$

Calculate the value of wye load.

$$\begin{aligned} Z_Y &= \frac{Z_{\Delta}}{3} \\ &= \frac{51 + j45}{3} \\ &= 17 + j15 \, \Omega \end{aligned}$$

The modified circuit is shown in Figure 2.

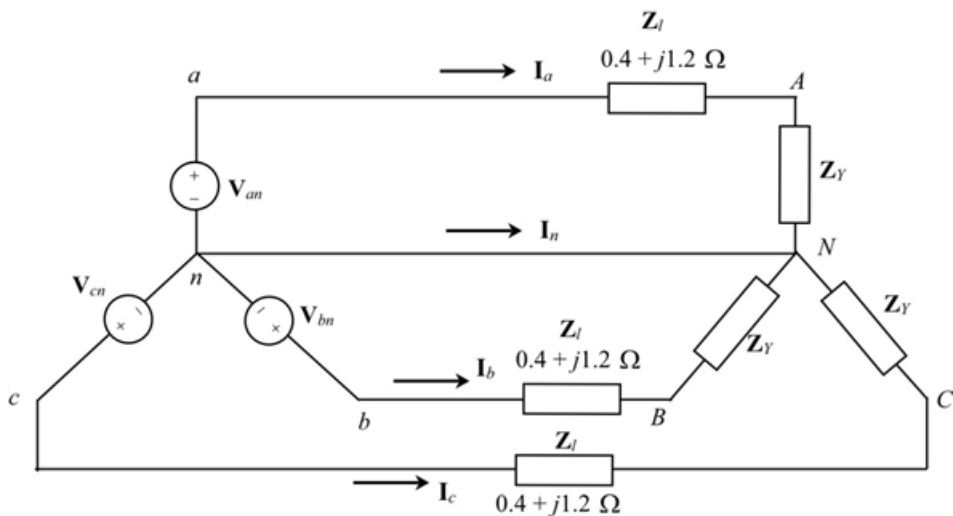


Figure 2

Draw the per phase equivalent circuit as shown in Figure 3.

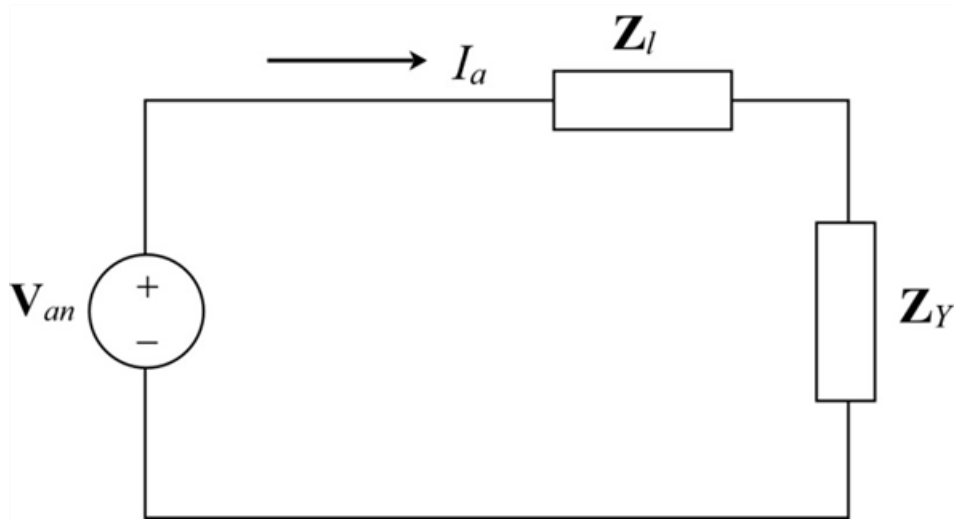


Figure 3

Step 3 of 4

Calculate the line current $\mathbf{I}_a$ from Figure 3.

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_l + \mathbf{Z}_Y}$$

Substitute $240\angle 0^\circ$ for $\mathbf{V}_{an}$, $0.4 + j1.2 \, \Omega$ for $\mathbf{Z}_l$, and $17 + j15 \, \Omega$ for $\mathbf{Z}_Y$.

$$\begin{aligned} \mathbf{I}_a &= \frac{240\angle 0^\circ}{0.4 + j1.2 + 17 + j15} \\ &= \frac{240\angle 0^\circ}{17.4 + j16.2} \\ &= \frac{240\angle 0^\circ}{23.77\angle 42.95^\circ} \\ &= 10.095\angle -42.95^\circ \text{ A} \end{aligned}$$

Calculate total complex power per phase delivered to the load, $\mathbf{S}$.

$$\begin{aligned} S_{ph} &= |\mathbf{I}_a|^2 \mathbf{Z}_Y \\ &= (10.095)^2 (17 + j15) \\ &= 1732.45 + j1528.63 \end{aligned}$$

Step 4 of 4

Calculate the total three phase complex power delivered to the load, $\mathbf{S}$.

$$\begin{aligned} S &= 3S_{ph} \\ &= 3(1732.45 + j1528.63) \\ &= 5197.36 + j4585.91 \text{ VA} \\ &= 5.197 + j4.586 \text{ kVA} \end{aligned}$$

Therefore, the total complex power delivered to the load is $\boxed{5.197 + j4.586 \text{ kVA}}$.