

Given $V_L = 208\text{V}$ and $Z_L = 30\angle 45^\circ\Omega$

Total complex power of the given circuit

$$S = 3S_p$$

$$S = \frac{3V_p^2}{Z_p^*}$$

We know that

$$V_p = \frac{V_L}{\sqrt{3}}$$

$$S = \frac{3\left(\frac{V_L}{\sqrt{3}}\right)^2}{Z_p^*}$$

$$S = \frac{V_L^2}{Z_p^*}$$

$$S = \frac{(208)^2}{30\angle 45^\circ}$$

$$S = 1442.13\angle -45^\circ \text{ VA}$$

We know that $P = S \cos \theta$

$$P = 1442.13 \cos(-45^\circ)$$

$$P = 1442.13(0.7071)$$

$$P = 1019.74$$

$$\boxed{P = 1.02\text{kW}}$$