

Problem

Design a problem to help other students better understand power in a balanced three-phase system.

Step-by-step solution

Step 1 of 2

Design a problem to help other students better understand power in a balanced three-phase system.

Although there are many ways to solve this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

A balanced wye load is connected to a 60-Hz three-phase source with $V_{ab} = 240 \angle 0^\circ \text{ V}$. The load has lagging $\text{pf} = 0.5$ and each phase draws 5 kW. (a) Determine the load impedance Z_Y . (b) Find I_a , I_b , and I_c .

Solution

$$(a) |V_{ab}| = \sqrt{3}V_p = 240 \longrightarrow V_p = \frac{240}{\sqrt{3}} = 138.56$$

$$V_{an} = V_p \angle -30^\circ$$

$$\text{pf} = 0.5 = \cos \theta \longrightarrow \theta = 60^\circ$$

$$P = S \cos \theta \longrightarrow S = \frac{P}{\cos \theta} = \frac{5}{0.5} = 10 \text{ kVA}$$

$$Q = S \sin \theta = 10 \sin 60 = 8.66$$

$$S_p = 5 + j8.66 \text{ kVA}$$

But

$$S_p = \frac{V_p^2}{Z_p^*} \longrightarrow Z_p^* = \frac{V_p^2}{S_p} = \frac{138.56^2}{(5 + j8.66) \times 10^3} = 0.96 - j1.663$$

$$Z_p = 0.96 + j1.663 \Omega$$

Step 2 of 2

$$(b) I_a = \frac{V_{an}}{Z_Y} = \frac{138.56 \angle -30^\circ}{0.96 + j1.6627} = \underline{72.17 \angle -90^\circ \text{ A}}$$

$$I_b = I_a \angle -120^\circ = \underline{72.17 \angle -210^\circ \text{ A}}$$

$$I_c = I_a \angle +120^\circ = \underline{72.17 \angle 30^\circ \text{ A}}$$