

Problem

A 4200-V, three-phase transmission line has an impedance of $4 + j \Omega$ per phase. If it supplies a load of 1 MVA at 0.75 power factor (lagging), find:

(a) the complex power

(b) the power loss in the line

(c) the voltage at the sending end

Step-by-step solution

Step 1 of 3

$$(A) \quad S = 1 \left[0.75 + j \sin(\cos^{-1} 0.75) \right] = 0.75 + j 0.6614 \text{ MVA} .$$

Step 2 of 3

$$\begin{aligned} (B) \quad \bar{S} &= 3V_p I_p^* \Rightarrow I_p^* = \frac{S}{3V_p} \\ &= \frac{(0.75 + j 0.6614) \times 10^6}{3 \times 4200} \\ &= 59.52 + j 52.49 \\ P_L &= |I_p|^2 R_L = (79.36)^2 (4) \\ &= 25.19 \text{ KW} . \end{aligned}$$

Step 3 of 3

$$\begin{aligned} (C) \quad V_s &= V_L + I_p (4 + j) \\ &= 4.4381 - j 0.21 \text{ KV} \\ &= 4.443 \angle -2.709^\circ \text{ KV} . \end{aligned}$$