

Problem

The total power measured in a three-phase system feeding a balanced wye-connected load is 12 kW at a power factor of 0.6 leading. If the line voltage is 440 V, calculate the line current I_L and the load impedance Z_Y .

Step-by-step solution

Step 1 of 6

Calculate the value of the line current I_L .

$$I_L = \frac{P}{\sqrt{3}V_L(\text{pf})}$$

Substitute 12 kW for P , 0.6 for pf and 440 V for V_p .

$$\begin{aligned} I_L &= \frac{12 \text{ k}}{\sqrt{3}(440)(0.6)} \\ &= \frac{12 \text{ k}}{457.26} \\ &= 26.24 \text{ A} \end{aligned}$$

Therefore, the value of the line current I_L is, 26.24 A.

[Comments \(1\)](#)



Anonymous

its I=P/V why multiply by the Pf ??

Step 2 of 6

Calculate the value of the power factor angle θ .

$$\theta = \cos^{-1}(\text{pf})$$

Substitute 0.6 for pf.

$$\begin{aligned} \theta &= \cos^{-1}(0.6) \\ &= 53.13^\circ \end{aligned}$$

Therefore, the value of the power factor angle is, 53.13° .

Step 3 of 6

Calculate the value of the apparent power S .

$$S = \frac{P}{\text{pf}}$$

Substitute 12 kW for P and 0.6 for pf.

$$\begin{aligned} S &= \frac{12 \text{ k}}{0.6} \\ &= 20 \text{ kW} \end{aligned}$$

Therefore, the value of the apparent power S is, 20 kW.

Step 4 of 6

Calculate the value of the reactive power Q .

$$Q = -S \sin \theta$$

Reactive power is negative since power factor is leading.

Substitute 53.13° for θ and 20 kW for S .

$$\begin{aligned} Q &= -(20 \text{ k})(\sin 53.13^\circ) \\ &= -(20 \text{ k})(0.8) \\ &= -16 \text{ kVAR} \end{aligned}$$

Therefore, the value of the reactive power is Q is, -16 kVAR.

Step 5 of 6

Consider the expression for the complex power S .

$$S = P + jQ$$

Substitute -16 kVAR for Q and 12 kW for P .

$$S = (12 \text{ k} - j16 \text{ k}) \text{ VA}$$

Therefore, the value of the apparent power S is, $(12 \text{ k} - j16 \text{ k}) \text{ VA}$.

Step 6 of 6

Consider the expression for the complex power

$$S = \frac{3(V_p)^2}{Z^*}$$

$$Z^* = \frac{3(V_p)^2}{S}$$

$$Z = \left[\frac{3(V_p)^2}{S} \right]^*$$

Substitute $(12 \text{ k} - j16 \text{ k}) \text{ VA}$ for S and 440 V for V_p .

$$\begin{aligned} Z &= \left[\frac{3(440)^2}{12 \text{ k} - j16 \text{ k}} \right]^* \\ &= \left[\frac{3(193600)}{12 \text{ k} - j16 \text{ k}} \right]^* \\ &= \left[\frac{580800}{12 \text{ k} - j16 \text{ k}} \right]^* \\ &= [17.424 - j23.232]^* \end{aligned}$$

$$Z = 17.424 + j23.232$$

Here Z represents the total value of the load impedance. To calculate the impedance per phase of the wye load, total impedance is to be divided by 3. That is,

$$\begin{aligned} Z_{ph} &= \frac{17.424 + j23.232}{3} \\ &= 5.808 + j7.744 \Omega \end{aligned}$$

Therefore, the value of the impedance per phase Z_{ph} is, $5.808 + j7.744 \Omega$.