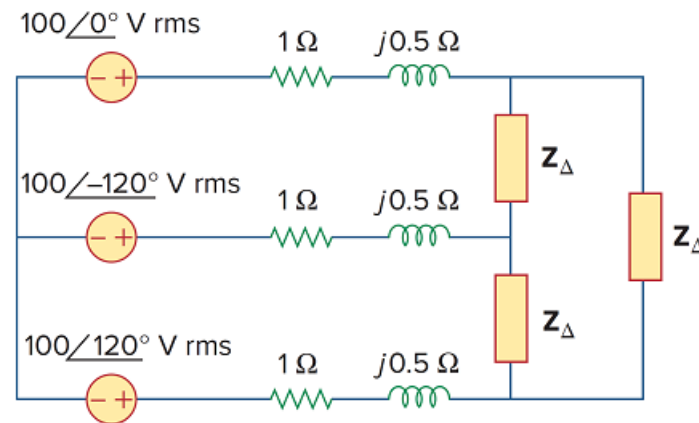


Problem

For the three-phase circuit in Fig. 12.59, find the average power absorbed by the delta-connected load with $\mathbf{Z}_{\Delta} = 21 + j24 \, \Omega$.

Figure 12.59



Step-by-step solution

Step 1 of 4

Refer to Figure 12.59 in the textbook.

Transform the Δ network into Y network.

Consider the load impedance $\mathbf{Z}_{\Delta} = 21 + j24 \, \Omega$.

Determine the equivalent load impedance of Y network $\mathbf{Z}_Y$.

Consider the equation for the $\mathbf{Z}_Y$.

$$\begin{aligned}\mathbf{Z}_Y &= \frac{\mathbf{Z}_{\Delta}}{3} \\ &= \frac{(21 + j24)}{3} \\ &= 7 + j8 \, \Omega\end{aligned}$$

Step 2 of 4

Determine the value of $\mathbf{I}_a$.

Consider the equation for $\mathbf{I}_a$.

$$\mathbf{I}_a = \frac{\mathbf{V}_{rms}}{\mathbf{Z}_A} \dots\dots (1)$$

Determine the value of $\mathbf{Z}_A$.

$$\begin{aligned}\mathbf{Z}_A &= (1 + j0.5) + (7 + j8) \\ &= 8 + j8.5 \, \Omega\end{aligned}$$

Replace $100\angle 0^\circ$ for $\mathbf{V}_{rms}$ and $(8 + j8.5) \, \Omega$ for $\mathbf{Z}_A$ in equation 1.

$$\begin{aligned}\mathbf{I}_a &= \frac{100\angle 0^\circ}{(8 + j8.5)} \\ &= 5.87 - j6.23 \, \text{A}\end{aligned}$$

Step 3 of 4

Determine the complex power.

$$\mathbf{S} = 3|\mathbf{I}_a|^2 (\mathbf{Z}_Y) \dots\dots (2)$$

Replace $7 + j8 \, \Omega$ for $\mathbf{Z}_Y$, and $5.87 - j6.23 \, \text{A}$ for $\mathbf{I}_a$ in equation 2.

$$\begin{aligned} \mathbf{S} &= 3|\mathbf{I}_a|^2 (\mathbf{Z}_Y) \\ &= 3(8.567)^2 (7 + j8 \, \Omega) \\ &= 220.18(7 + j8) \\ &= 1541.26 + j1761.44 \end{aligned}$$

Step 4 of 4

Determine the average power absorbed by load.

Consider the equation for average power.

$$P = \text{Re}(\mathbf{S}) \dots\dots (3)$$

Consider the real part of complex power.

$$\begin{aligned} P &= \text{Re}(\mathbf{S}) \\ &= 1541.26 \, \text{W} \end{aligned}$$

Therefore, the average power absorbed by the load is 1541.26 W.