

Problem

The following three parallel-connected three-phase loads are fed by a balanced three-phase source:

Load 1: 250 kVA, 0.8 pf lagging

Load 2: 300 kVA, 0.95 pf leading

Load 3: 450 kVA, unity pf

If the line voltage is 13.8 kV, calculate the line current and the power factor of the source. Assume that the line impedance is zero.

Step-by-step solution

Step 1 of 1

$$Pf = 0.8 \text{ [Lagging]} \Rightarrow \theta = \cos^{-1}(0.8) = 36.87^\circ$$

$$S_1 = 250 \angle 36.87^\circ = 200 + j150 \text{ KVA}$$

$$Pf = 0.95 \text{ [Leading]} \Rightarrow \theta = \cos^{-1}(0.95) = -18.19^\circ$$

$$S_2 = 300 \angle -18.9^\circ = 285 - j93.65 \text{ KVA}$$

$$Pf = 1.0 \Rightarrow \theta = \cos^{-1}(1) = 0^\circ$$

$$S_3 = 450 \text{ KVA}$$

$$S_T = S_1 + S_2 + S_3 = 935 + j56.35$$

$$= 936.7 \angle 3.45 \text{ KVA}$$

$$|S_T| = \sqrt{3} V_L I_L$$

$$I_L = \frac{936.7 \times 10^3}{\sqrt{3} (13.8 \times 10^3)} = 39.19 \text{ Arms}$$

$$Pf = \cos \theta = \cos(3.45^\circ) = 0.9982 \text{ [Lagging]} .$$