

Problem

A balanced, positive-sequence wye-connected source has

$\mathbf{V}_{an} = 240 \angle 0^\circ \text{ V rms}$ and supplies an unbalanced delta-connected load via a

transmission line with impedance $2 + j3 \Omega$ per phase.


(a) Calculate the line currents if $\mathbf{Z}_{AB} = 40 + j15 \Omega$, $\mathbf{Z}_{BC} = 60 \Omega$, $\mathbf{Z}_{CA} = 18 - j12 \Omega$.

(b) Find the complex power supplied by the source.

Step-by-step solution

Step 1 of 4

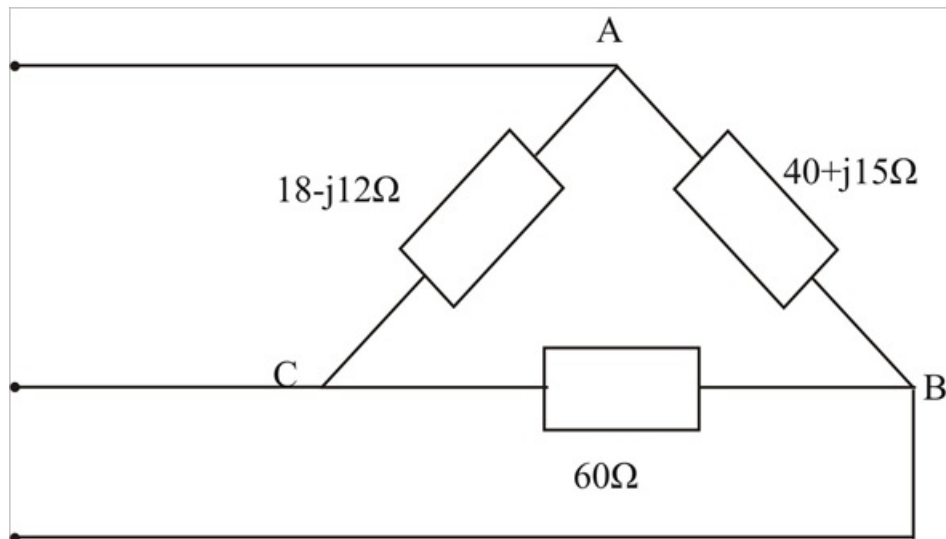(A) We first convert the delta load to its equivalent WYE – load as shown below.



Step 2 of 4

$$\mathbf{Z}_A = \frac{(40 + j15)(18 - j12)}{118 + j3} = 7.577 - j1.923$$

$$\mathbf{Z}_B = \frac{60(40 + j15)}{118 + j3} = 20.52 + j7.105$$

$$\mathbf{Z}_C = \frac{60(18 - j12)}{118 + j3} = 8.992 - j6.3303$$

The system becomes that shown below.

We apply KVL to the loops.

For Mesh 1,

$$-240 + 240 \angle -120^\circ + I_1(2\mathbf{Z}_1 + \mathbf{Z}_A + \mathbf{Z}_B) - I_2(\mathbf{Z}_B + \mathbf{Z}_1) = 0$$

$$\text{Or, } (32.097 + j11.13)I_1 - (22.52 + j10.105)I_2 = 360 + j20.785 \rightarrow (1)$$

Step 3 of 4

For Mesh 2,

$$240 \angle 120^\circ - 240 \angle -120^\circ - I_1(Z_B + Z_C) + I_2(2Z_1 + Z_B + Z_C) = 0$$

$$-(22.52 + j10.105)I_1 + (33.51 + 56.775)I_2 = -j415.69 \rightarrow (2)$$

Solving (1) & (2) gives,

$$I_1 = 23.75 - j5.328$$

$$I_2 = 15.165 - j11.89$$

$$I_{aA} = I_1 = 24.34 \angle -12.64^\circ \text{ A}$$

$$I_{bB} = I_2 - I_1 = 10.81 \angle -142.6^\circ \text{ A}$$

$$I_{cC} = -I_2 = 19.27 \angle 141.9^\circ \text{ A}$$

Step 4 of 4

$$(B) \overline{S}_a = (240 \angle 0^\circ)(24.34 \angle 12.64^\circ) = 5841.6 \angle 12.64^\circ$$

$$\overline{S}_b = (240 \angle -120^\circ)(10.81 \angle 42.6^\circ) = 2834.4 \angle 22.6^\circ$$

$$\overline{S}_c = (240 \angle 120^\circ)(19.207 \angle -141.9^\circ) = 4624.8 \angle -21.9^\circ$$

$$\overline{S} = \overline{S}_a + \overline{S}_b + \overline{S}_c$$

$$= 12.386 + j0.58 \text{ KVA}$$

$$= 12.4 \angle 2.54^\circ \text{ KVA}$$