

Problem

A four-wire wye-wye circuit has

$$\begin{aligned} \mathbf{V}_{an} &= 220\angle 120^\circ, & \mathbf{V}_{bn} &= 220\angle 0^\circ \\ \mathbf{V}_{cn} &= 220\angle -120^\circ \text{ V} \end{aligned}$$

If the impedances are


$$\begin{aligned} \mathbf{Z}_{AN} &= 20\angle 60^\circ, & \mathbf{Z}_{BN} &= 30\angle 0^\circ \\ \mathbf{Z}_{cn} &= 40\angle 30^\circ \Omega \end{aligned}$$

find the current in the neutral line.

Step-by-step solution

Step 1 of 5

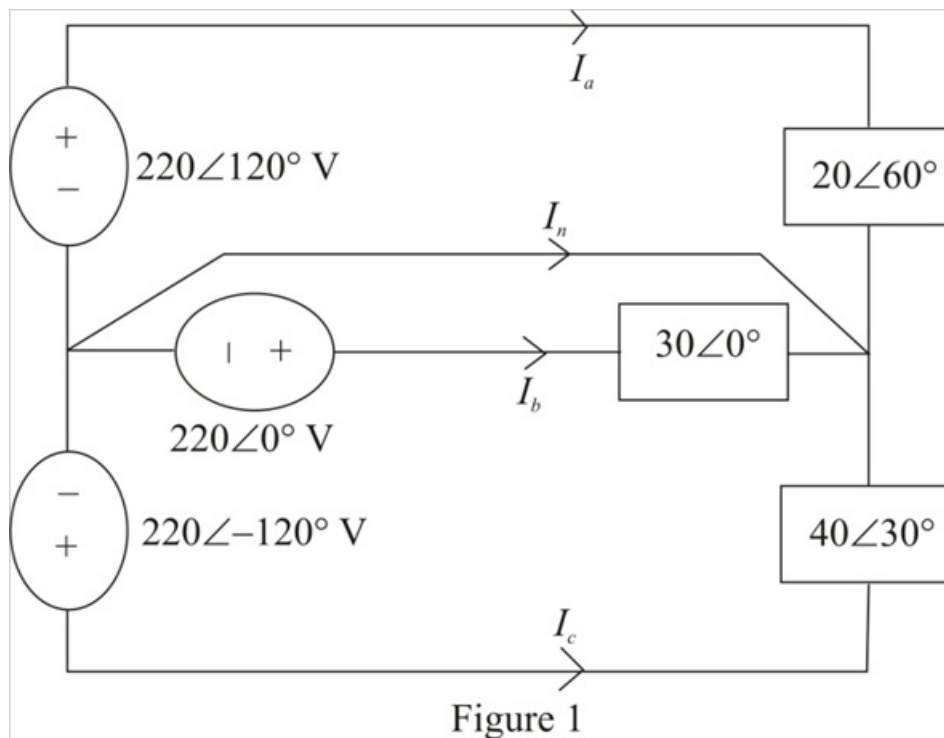Consider the circuit diagram shown in Figure 1.



Step 2 of 5

Calculate the value of the current I_a .

$$\begin{aligned} I_a &= \frac{220\angle 120^\circ}{20\angle 60^\circ} \\ &= 11\angle 60^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_a is, $11\angle 60^\circ \text{ A}$.

Step 3 of 5

Calculate the value of the current I_b .

$$\begin{aligned} I_b &= \frac{220\angle 0^\circ}{30\angle 0^\circ} \\ &= 7.33\angle 0^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_b is, $7.33\angle 0^\circ \text{ A}$.

Step 4 of 5

Calculate the value of the current I_c .

$$\begin{aligned} I_c &= \frac{220\angle -120^\circ}{40\angle 30^\circ} \\ &= 5.5\angle -150^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_c is, $5.5\angle -150^\circ \text{ A}$.

Step 5 of 5

Calculate the value of the current I_n .

$$I_n = -(I_a + I_b + I_c)$$

Substitute $11\angle 60^\circ \text{ A}$ for I_a , $7.33\angle 0^\circ \text{ A}$ for I_b and $5.5\angle -150^\circ \text{ A}$ for I_c .

$$\begin{aligned} I_n &= -(11\angle 60^\circ + 7.33\angle 0^\circ + 5.5\angle -150^\circ) \\ &= -(10.54\angle 40^\circ) \\ &= 10.54\angle -140^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_n is, $10.54\angle -140^\circ \text{ A}$.