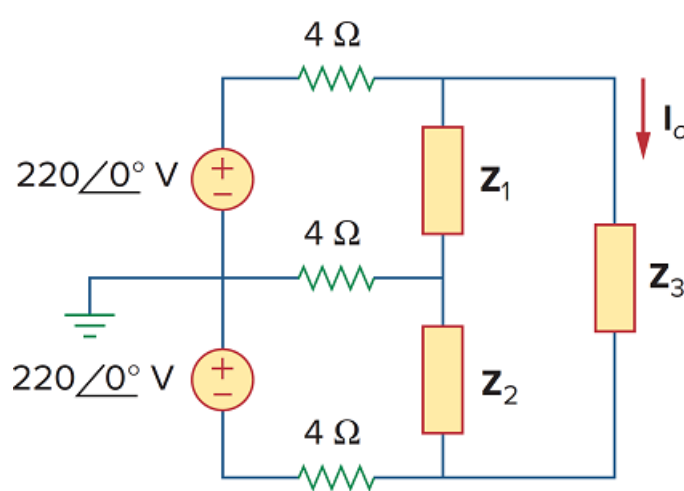


Problem

Use *PSpice* or *MultiSim* to determine I_o in the single-phase, three-wire circuit of Fig. 12.66. Let $Z_1 = 15 - j10 \, \Omega$, $Z_2 = 30 + j20 \, \Omega$, and $Z_3 = 12 + j5 \, \Omega$.

Figure 12.66



Step-by-step solution

Step 1 of 2

The schematics is shown below. IPRINT is inserted to give I_o . We select Total points = 1, Start frequency = 0.1892, End frequency = 0.1892 in the sweep box, upon simulation, output file includes,

Frequency	IN(V_PRINT 4)	IP(V_PRINT 4)
$1.592 E - 01$	$1.421 E + 00$	$-1.355 E + 02$

Step 2 of 2

From which,

$$I_0 = 1.421 \angle -135.5^\circ \text{ A} .$$

