


## Problem

Use *PSpice* or *MultiSim* to find currents  $I_{aA}$  and  $I_{AC}$  in the unbalanced three-phase system shown in Fig. 12.69. Let

$$Z_l = 2 + j, \quad Z_1 = 40 + j20 \, \Omega,$$

$$Z_2 = 50 - j30 \, \Omega, \quad Z_3 = 25 \, \Omega$$

Figure 12.69

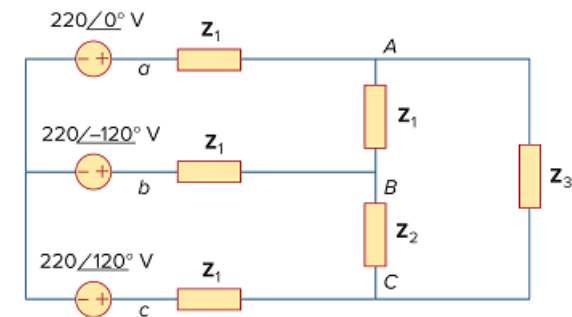

## Step-by-step solution

## Step 1 of 4

Let  $\omega = 1$ ,


So that,

$$L = \frac{X}{\omega} = 204$$

And,

$$C = \frac{1}{\omega X} = 0.0333 \text{ F}$$

## Step 2 of 4

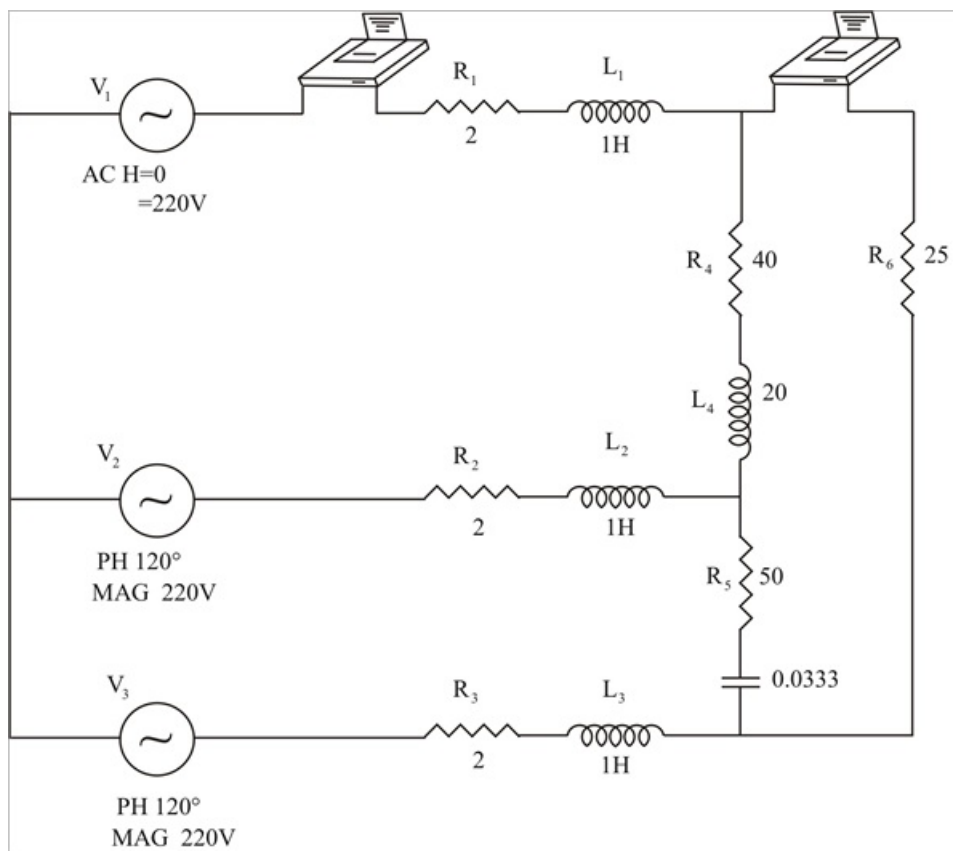

**Step 3** of 4

|                  |                      |                     |
|------------------|----------------------|---------------------|
| <i>Frequency</i> | <i>1 M(V_PRINT1)</i> | <i>IP(V_PRINT1)</i> |
| $1.592 E-01$     | $1.867 E+01$         | $1.589 E+02$        |
| <i>Frequency</i> | <i>1 M(V_PRINT2)</i> | <i>IP(V_PRINT2)</i> |
| $1.592 E-01$     | $1.238 E+01$         | $1.441 E+02$        |

**Step 4** of 4

From the output file, the required currents are,

$$I_{aA} = 18.60 \angle 158.9^\circ \text{ A}$$

$$I_{AC} = 12.38 \angle 144.1^\circ \text{ A} .$$