

Problem

A certain store contains three balanced three-phase loads. The three loads are:

Load 1: 16 kVA at 0.85 pf lagging

Load 2: 12 kVA at 0.6 pf lagging

Load 3: 8 kW at unity pf

The line voltage at the load is 208 V rms at 60 Hz, and the line impedance is $0.4 + j0.8 \Omega$. Determine the line current and the complex power delivered to the loads.

Step-by-step solution

Step 1 of 7

Substitute 31.79° for θ_1 and 16 kVA for S_1 in equation (1).

$$\begin{aligned}\overline{S}_1 &= (16000)\cos(31.79^\circ) + j(16000)\sin(31.79^\circ) \\ &= (16000)(0.849) + j(16000)(0.526) \\ &= 13.58 \text{ kVA} + j8.41 \text{ kVA} \\ &= (13.6 + j8.43) \text{ kVA}\end{aligned}$$

Therefore, the complex power delivered to the load 1 is $(13.6 + j8.43) \text{ kVA}$.

Step 2 of 7

Write the formula for complex power to load 2.

$$\overline{S}_2 = S_2 \cos \theta_2 + jS_2 \sin \theta_2 \dots\dots (2)$$

Where,

The power factor, $\cos \theta_2$

For load 2, the pf is 0.6. Therefore,

$$\begin{aligned}\cos \theta_2 &= 0.6 \\ \theta_2 &= \cos^{-1}(0.6) \\ \theta_2 &= 53.13^\circ\end{aligned}$$

Step 3 of 7

Substitute 53.13° for θ_2 and 12 kVA for S_2 in equation (2).

$$\begin{aligned}\overline{S}_2 &= (12000)\cos(53.13^\circ) + j(12000)\sin(53.13^\circ) \\ &= (12000)(0.6) + j(12000)(0.799) \\ &= 7.2 \text{ kVA} + j9.6 \text{ kVA} \\ &= (7.2 + j9.6) \text{ kVA}\end{aligned}$$

Therefore, the complex power delivered to the load 2 is $(7.2 + j9.6) \text{ kVA}$.

Step 4 of 7

Write the formula for complex power to load 3.

$$\overline{S}_3 = S_3 \cos \theta_3 + j S_3 \sin \theta_3 \dots\dots (3)$$

Where,

The power factor, $\cos \theta_3$

For load 3, the pf is 1. Therefore,

$$\cos \theta_3 = 1$$

$$\theta_3 = \cos^{-1}(1)$$

$$\theta_3 = 0^\circ$$

Step 5 of 7

Substitute 0° for θ_3 and 8 kVA for S_3 in equation (3).

$$\begin{aligned}\overline{S}_3 &= (8000) \cos(0^\circ) + j(8000) \sin(0^\circ) \\ &= (8000)(1) + j(8000)(0) \\ &= 8 \text{ kVA} + j0 \text{ kVA} \\ &= (8 + j0) \text{ kVA}\end{aligned}$$

Therefore, the complex power delivered to the load 2 is $(8 + j0) \text{ kVA}$.

Step 6 of 7

Determine the total complex power of the loads by adding the three complex powers.

$$\begin{aligned}S_p &= \overline{S}_1 + \overline{S}_2 + \overline{S}_3 \\ &= [(13.6 + j8.43) + (7.2 + j9.6) + (8 + j0)] \text{ kVA} \\ &= 28.8 + j18.03 \text{ kVA}\end{aligned}$$

The source voltage, $V_{ab} = 208 \text{ V rms}$

Calculate the value of the V_{an} .

$$\begin{aligned}V_{an} &= \frac{V_{ab} \angle -30^\circ}{\sqrt{3}} \\ &= \frac{208 \angle -30^\circ}{\sqrt{3}} \\ &= 120.08 \angle -30^\circ\end{aligned}$$

It is known that the complex power is,

$$S_p = V_p I_p^* \dots\dots (4)$$

Where,

The current $I_p = I_L$

Rearrange the equation (4) for I_p^* .

$$\begin{aligned}I_p^* &= \frac{S_p}{V_p} \\ &= \frac{28800 + j18030}{(3)(120.08)} \\ &= 79.95 + j50.05 \text{ A}\end{aligned}$$

$$\begin{aligned}I_L &= 79.95 - j50.05 \text{ A} \\ &= 94.32 \angle 32.05^\circ \text{ A}\end{aligned}$$

Step 7 of 7

Now, assume the positive phase rotation. But the voltage $\mathbf{V}_{ab} = 208\angle 0^\circ$ then

$\mathbf{V}_{an} = 120.08\angle -30^\circ \text{ V}$. Then which yields,

$$\mathbf{I}_a = 94.32\angle -30^\circ - 32.05^\circ \text{ A}$$

$$= 94.32\angle -62.05^\circ \text{ A}$$

$$\mathbf{I}_b = 94.32\angle -120^\circ - 30^\circ - 32.05^\circ \text{ A}$$

$$= 94.32\angle 177.95^\circ \text{ A}$$

$$\mathbf{I}_c = 94.32\angle 120^\circ - 30^\circ - 32.05^\circ \text{ A}$$

$$= 94.32\angle 57.95^\circ \text{ A}$$

Therefore, the line currents $\mathbf{I}_a, \mathbf{I}_b, \mathbf{I}_c$ are $94.32\angle -62.05^\circ \text{ A}$, $94.32\angle 177.95^\circ \text{ A}$ and

$94.32\angle 57.95^\circ \text{ A}$ respectively.