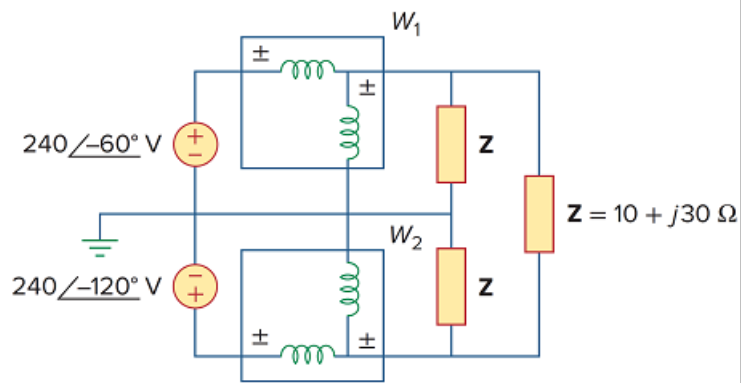


Problem

For the circuit displayed in Fig. 12.74, find the wattmeter readings.


Figure 12.74



Step-by-step solution

Step 1 of 3

Consider the circuit shown below.

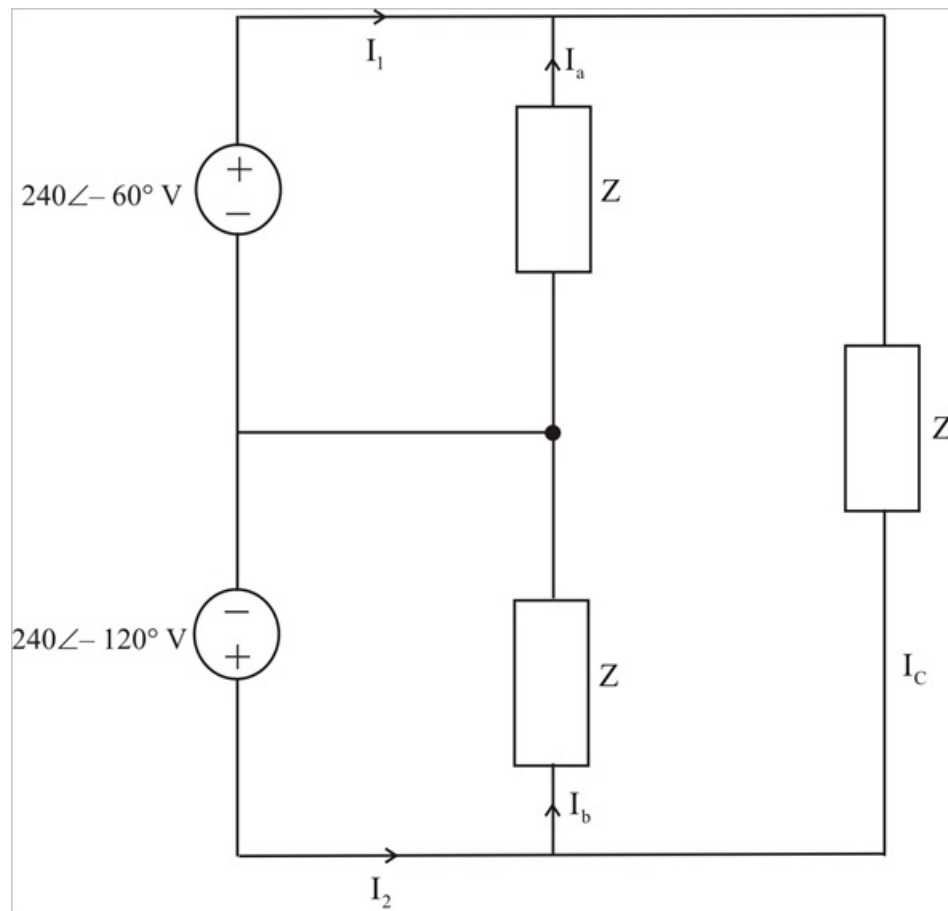

Step 2 of 3

$$Z = 10 + j30 = 31.62 \angle 71.57^\circ$$

$$I_a = \frac{240 \angle -60^\circ}{31.62 \angle 71.57^\circ} = 7.59 \angle -131.57^\circ$$

$$I_b = \frac{240 \angle -120^\circ}{3.62 \angle 71.57^\circ} = 7.59 \angle -191.57^\circ$$

Step 3 of 3

$$I_c Z + 240 \angle -60^\circ - 240 \angle -120^\circ = 0$$

$$I_c = I_c = \frac{-240}{31.62 \angle 71.57^\circ} = 7.59 \angle 108.43^\circ$$

$$I_1 = I_a - I_c = 13.146 \angle -101.57^\circ$$

$$I_2 = I_b - I_c = 13.146 \angle 138.43^\circ$$

$$P_1 = R_e [V_1 I_1^*]$$

$$= R_e [(240 \angle -60^\circ) (13.146 \angle 101.57^\circ)]$$

$$= 2360 \text{ W}$$

$$P_2 = R_e [V_2 I_2^*]$$

$$= R_e [(240 \angle -120^\circ) (13.146 \angle -138.43^\circ)]$$

$$= -632.8 \text{ W} .$$