

Problem

Design a three-phase heater with suitable symmetric loads using wye-connected pure resistance. Assume that the heater is supplied by a 240-V line voltage and is to give 27 kW of heat.

Step-by-step solution

Step 1 of 1

$$\text{Let } Z_y = R$$

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{240}{\sqrt{3}}$$

$$= 138.56 \text{ V}$$

$$P = V_p I_p = \frac{27}{2} = 9 \text{ KW} = \frac{V_p^2}{R}$$

$$\Rightarrow R = \frac{V_p^2}{P} = \frac{(138.56)^2}{9000}$$

$$= 2.133 \text{ } \Omega$$

Thus,

$$Z_y = 2.133 \text{ } \Omega .$$