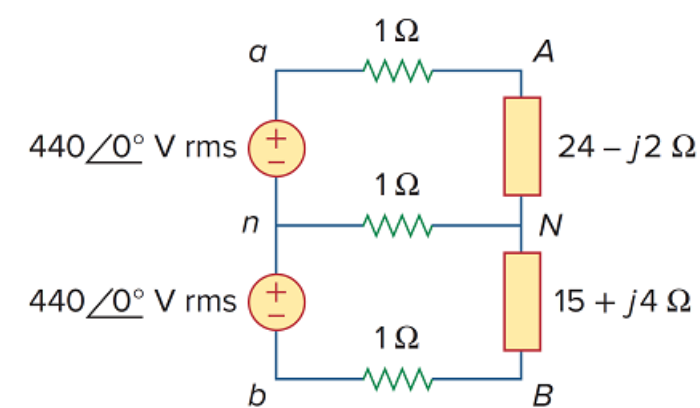


Problem

For the single-phase three-wire system in Fig. 12.77, find currents I_{aA} , I_{bB} , and I_{nN} .

Figure 12.77




Step-by-step solution

Step 1 of 6

Refer to Figure 12.77 in the text book.

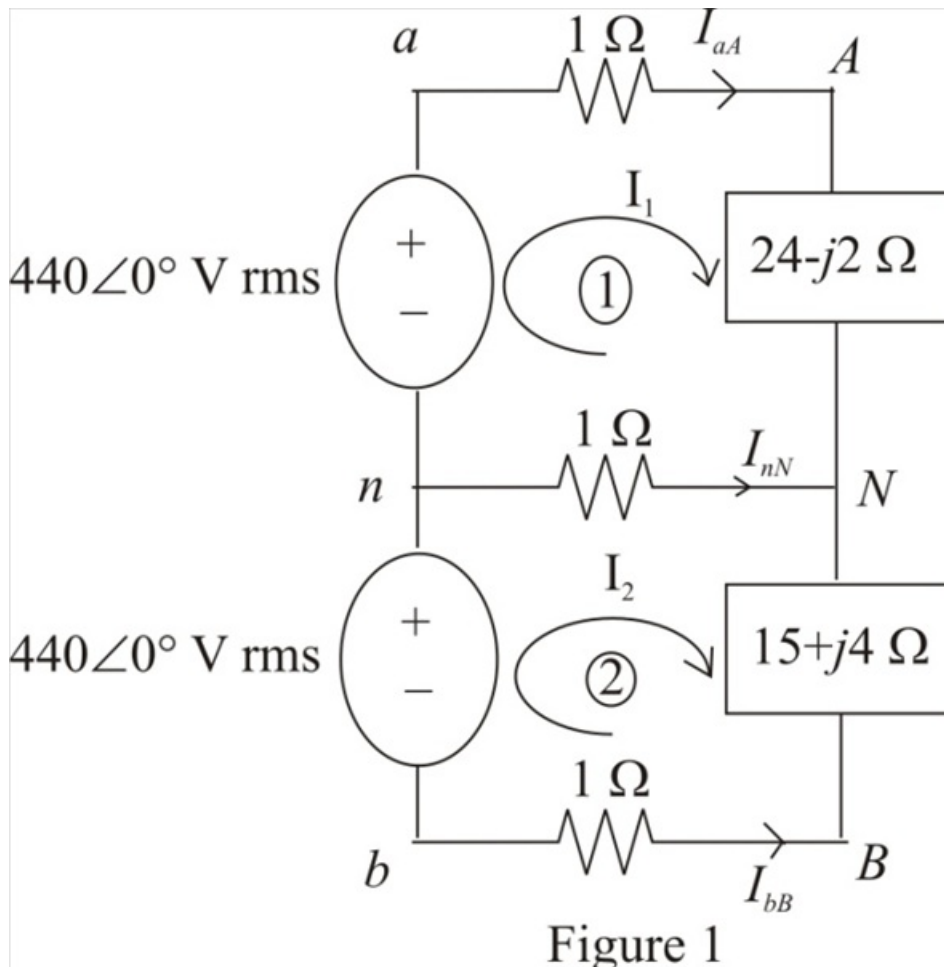Identify the loops and currents in the circuit diagram shown in Figure 1.



Step 2 of 6

Apply Kirchhoff's Voltage Law in Loop-1.

$$-440\angle 0^\circ + I_1(1) + I_1(24 - j2) + (I_1 - I_2)(1) = 0$$

$$I_1(1 + 24 - j2 + 1) - I_2(1) = 440\angle 0^\circ$$

$$I_1(26 - j2) - I_2 = 440\angle 0^\circ$$

$$I_2 = 440\angle 0^\circ + I_1(26 - j2) \dots\dots (1)$$

Therefore, the expression for the current I_2 is, $440\angle 0^\circ + I_1(26 - j2)$.

Step 3 of 6

Apply Kirchhoff's Voltage Law in Loop-2.

$$-440\angle 0^\circ + (I_2 - I_1)(1) + I_2(15 + j4) + I_2(1) = 0$$

$$I_2(1 + 15 + j4 + 1) - I_1(1) = 440\angle 0^\circ$$

$$I_2(17 + j4) - I_1 = 440\angle 0^\circ$$

Substitute $440\angle 0^\circ + I_1(26 - j2)$ for I_2 .

$$[440\angle 0^\circ + I_1(26 - j2)](17 + j4) - I_1 = 440\angle 0^\circ$$

$$[440\angle 0^\circ + I_1(26.08\angle -4.4^\circ)](17.46\angle 13.24^\circ) - I_1 = 440\angle 0^\circ$$

$$7682.4\angle 13.24^\circ + I_1(455.36\angle 8.84^\circ) - I_1 = 440\angle 0^\circ$$

$$7682.4\angle 13.24^\circ + I_1(454.37\angle 8.86^\circ) = 440\angle 0^\circ$$

$$I_1(454.37\angle 8.86^\circ) = 440\angle 0^\circ - 7682.4\angle 13.24^\circ$$

$$I_1(454.37\angle 8.86^\circ) = 7254.8\angle -165.96^\circ$$

$$I_1 = \frac{7254.8\angle -165.96^\circ}{454.37\angle 8.86^\circ}$$

$$I_1 = 16\angle -174.82^\circ \text{ A}$$

Therefore, the value of the current I_1 is, $16\angle -174.82^\circ \text{ A}$.

The current I_1 represents the current I_{ad} . Therefore, the value of the current I_{ad} is,

$$\boxed{16\angle -174.82^\circ \text{ A}}.$$

Step 4 of 6

Recall equation (1).

$$I_2 = 440\angle 0^\circ + I_1(26 - j2)$$

Substitute $16\angle -174.82^\circ \text{ A}$ for I_1 .

$$I_2 = 440\angle 0^\circ + (16\angle -174.82^\circ)(26 - j2)$$

$$= 440\angle 0^\circ + (16\angle -174.82^\circ)(26.08\angle -4.4^\circ)$$

$$= 440\angle 0^\circ + 417.28\angle -179.22^\circ$$

$$= 23.46\angle -14.02^\circ \text{ A}$$

Therefore, the value of the current I_2 is $23.46\angle -14.02^\circ \text{ A}$.

Step 5 of 6

Calculate the value of the current I_{bb} .

$$I_{bb} = -I_2$$

Substitute $23.46\angle -14.02^\circ \text{ A}$ for I_2 .

$$\begin{aligned} I_{bb} &= -23.46\angle -14.02^\circ \\ &= 23.46\angle 165.98^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_{bb} is, $23.46\angle 165.98^\circ \text{ A}$.

Step 6 of 6

Calculate the value of the current I_{nN} .

$$I_{nN} = I_2 - I_1$$

Substitute $23.46\angle -14.02^\circ \text{ A}$ for I_2 and $16\angle -174.82^\circ \text{ A}$ for I_1 .

$$\begin{aligned} I_{nN} &= 23.46\angle -14.02^\circ - 16\angle -174.82^\circ \\ &= 38.93\angle -6.25^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current I_{nN} is, $38.93\angle -6.25^\circ \text{ A}$.