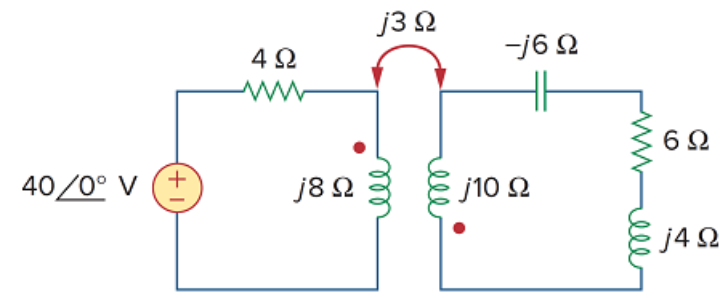


Problem

Find the input impedance of the circuit in Fig. 13.25 and the current from the voltage source.

Figure 13.25



Step-by-step solution

Step 1 of 3

Figure 1

Step 2 of 3

Write the expression for impedance $\mathbf{Z}_{in}$ seen by the voltage source.

$$\begin{aligned}
 \mathbf{Z}_{in} &= \frac{\mathbf{V}_1}{\mathbf{I}_1} \\
 &= R_1 + j\omega L + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \\
 &= R_1 + j\omega L + \frac{X_M^2}{R_2 + j\omega L_2 + Z_L} \\
 \mathbf{Z}_{in} &= 4 + j8 + \frac{3^2}{j10 - j6 + 6 + j4} \\
 &= 4 + j8 + \frac{9}{6 + j8} \\
 &= 4 + j8 + 0.54 - j0.72 \\
 &= 4.57 + j7.28
 \end{aligned}$$

$$\mathbf{Z}_{in} = 8.58 \angle 58.05^\circ \Omega$$

So input impedance $\mathbf{Z}_{in}$ is $\boxed{8.58 \angle 58.05^\circ \Omega}$

Step 3 of 3

Calculate the value of the current $\mathbf{I_1}$.

Write the expression for input impedance $\mathbf{Z_{in}}$.

$$\mathbf{Z_{in}} = \frac{\mathbf{V_1}}{\mathbf{I_1}}$$

$$8.58\angle 58.05^\circ = \frac{40\angle 0^\circ}{\mathbf{I_1}}$$

$$\mathbf{I_1} = \frac{40\angle 0^\circ}{8.58\angle 58.05^\circ}$$

$$\mathbf{I_1} = 4.602\angle -58.05^\circ$$

The current $\mathbf{I_1}$ from the voltage source is $\boxed{4.602\angle -58.05^\circ \text{ A}}$.