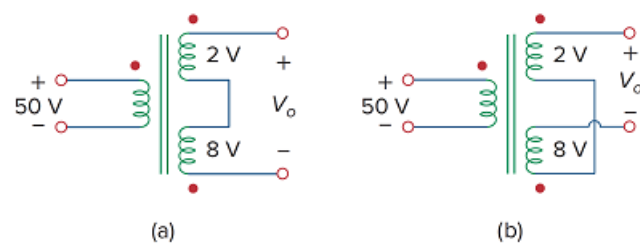


Problem

If the three-winding transformer is connected as in Fig. 13.71(b), the value of the output voltage V_o is:

- (a) 10
- (b) 6
- (c) -6
- (d) -10

Figure 13.71



Step-by-step solution

Step 1 of 1

13.8

A .