

Chapter 13, Problem 9RQ

Problem

In order to match a source with internal impedance of $500\ \Omega$ to a $15\text{-}\Omega$ load, what is needed is:

- (a) step-up linear transformer
- (b) step-down linear transformer
- (c) step-up ideal transformer
- (d) step-down ideal transformer
- (e) autotransformer

Step-by-step solution

Step 1 of 1

13.9

D .