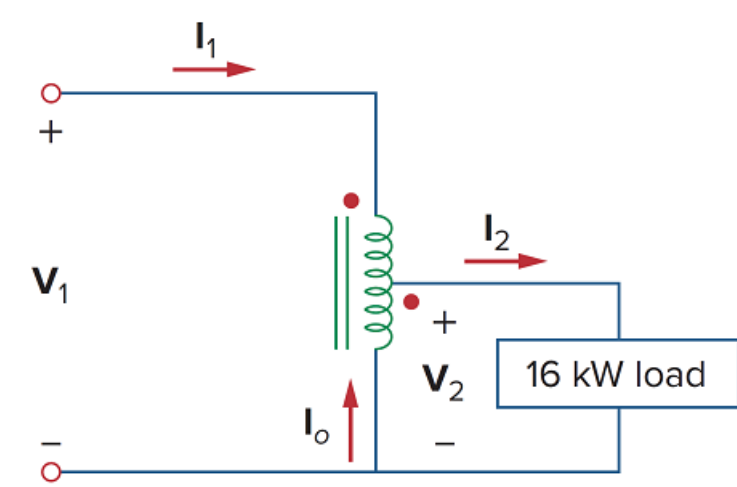


Problem

In the autotransformer circuit of Fig. 13.45, find currents I_1 , I_2 , and I_o . Take $V_1 = 8$ kV, $V_2 = 2$ kV.

Figure 13.45



Step-by-step solution

Step 1 of 4

Refer to Figure 13.45 from the textbook.

Write the expression for the power delivered to the load, p_2 .

$$p_2 = V_2 I_2 \dots\dots (1)$$

Here,

V_2 is the secondary side voltage of the auto transformer,

I_2 is the secondary side current of the auto transformer.

Step 2 of 4

Substitute 2 kV for V_2 and 16 kW for p_2 in equation (1).

$$16 \times 10^3 = (2 \times 10^3) I_2$$

$$I_2 = \frac{16}{2}$$

$$I_2 = 8 \text{ A}$$

Step 3 of 4

Since the power at both the ends of the transformer is same.

Thus,

$$P_1 = P_2$$

$$V_1 I_1 = V_2 I_2$$

Substitute 16 kV for V_1 , 2 kV for V_2 and 8 A for I_2 .

$$(8 \times 10^3) I_1 = (2 \times 10^3)(8)$$

$$I_1 = \frac{16 \times 10^3}{8 \times 10^3}$$

$$I_1 = 2 \text{ A}$$

Step 4 of 4

Calculate the current, I_o .

Apply Kirchhoff's Current Law at the meeting point of I_1 , I_2 and I_o .

$$I_o + I_1 - I_2 = 0$$

$$I_o = I_2 - I_1$$

Substitute 2 A for I_1 and 8 A for I_2 .

$$I_o = 8 - 2$$

$$= 6 \text{ A}$$

Therefore, the currents, I_1 , I_2 and I_o are 2 A, 8 A and 6 A respectively.