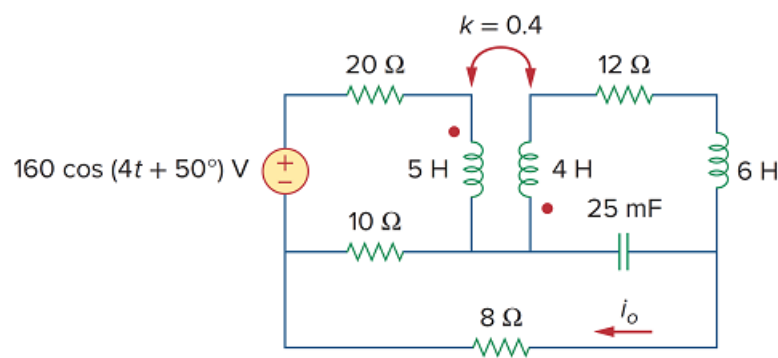


Problem

Find i_o in the circuit of Fig. 13.55, using PSpice.

Figure 13.55



Step-by-step solution

Step 1 of 6


Step 1:

Select draw / get new part and type XFRM_LINEAR.

Click ok and place the XFRM_LINEAR symbol on the schematic, as shown in below figures (2) and double click on XFRM_LINEAR device and set coupling = 0.4,

L_1 _value = 5 and L_2 _value = 4 as shown below.


Step 2 of 6

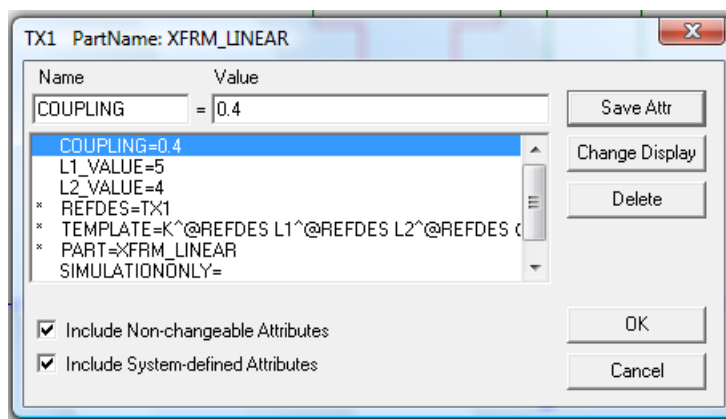

Step 3 of 6

Step 2:

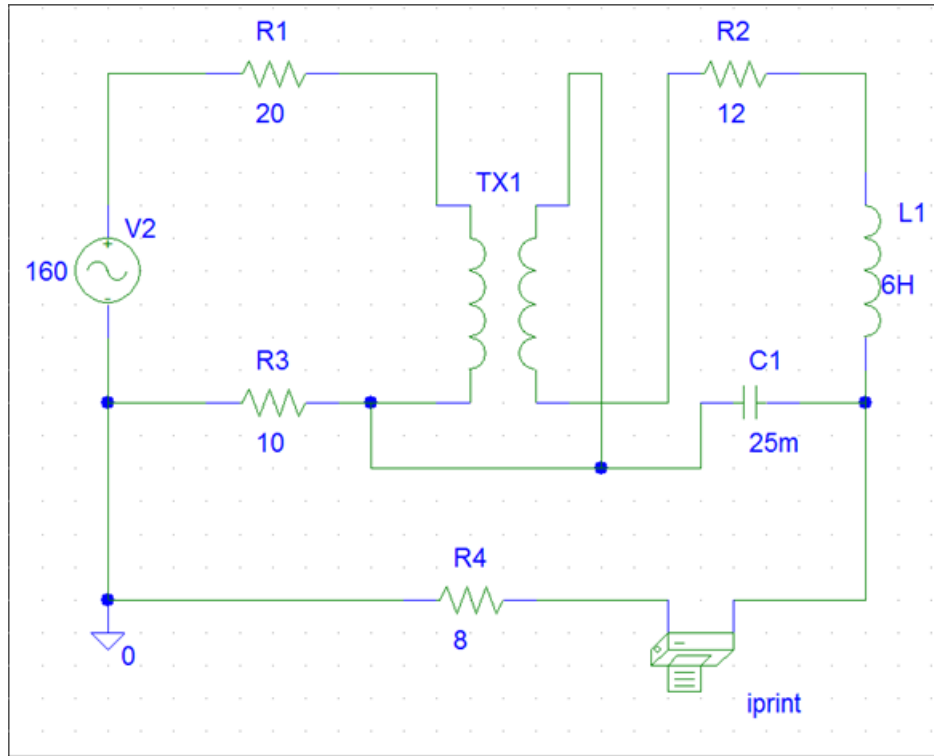After making all connections by using *PSpice* given circuit is as below



Step 4 of 6

Step 3:

Double click on VAC voltage source and set $DC = 0V$, $ACMAG = 160$ and $ACPHASE = 50$ and double click on IPRINT and set $AC = yes$, $MAG = yes$ and $PHASE = yes$.

Step 5 of 6

Step 4:

$$\omega = 4 \text{ rad/sec}$$

$$2\pi f = 4$$

$$f = \frac{4}{2\pi}$$

$$f = 0.63662 \text{ Hz}$$

Go to analysis / set up and select AC sweep / linear and enter total points = 1, start frequency = 0.63662 Hz end frequency = 0.63662 Hz .

Step 6 of 6

Step 5:

We select analysis / simulate it. The output file induces.

FREQ IM(V_PRINT1) IP(V_PRINT1)

6.366E-01 2.011E+00 6.851E+01