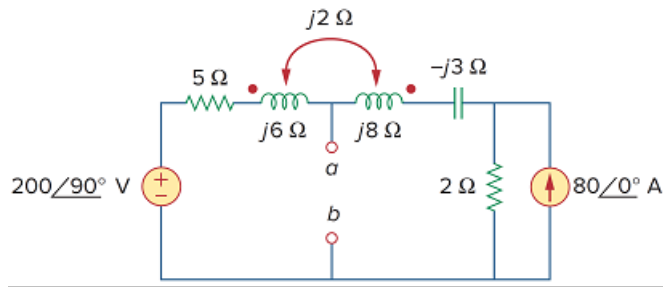


Problem

Obtain the Thevenin equivalent circuit for the circuit in Fig. 13.83 at terminals a - b .

Figure 13.83



Step-by-step solution

Step 1 of 8

Refer to the circuit diagram in Figure 13.83 in the textbook.

Convert the current source $80\angle 0^\circ$ A into voltage source using source transformation.

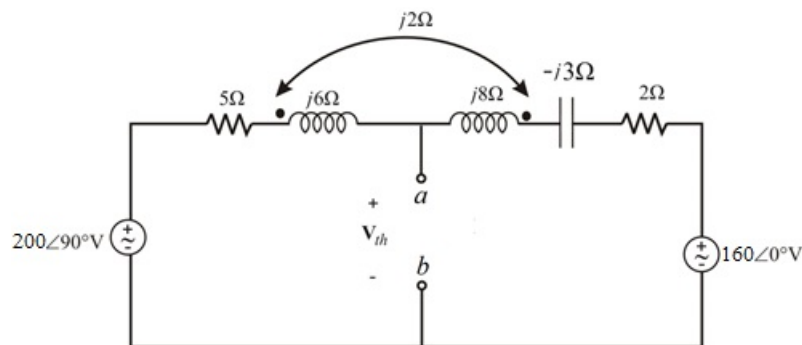


Figure 1

Step 2 of 8

Apply Kirchhoff's voltage law around outer loop.

$$-200\angle 90^\circ + 5\mathbf{I} + (j6 - j8 - j4)\mathbf{I} + (-j3 + 2)\mathbf{I} + 160\angle 0^\circ = 0$$

$$(7 + j7)\mathbf{I} + 160 - j200 = 0$$

Solve for $\mathbf{I}$.

$$\mathbf{I} = -\frac{160 - j200}{7 + j7}$$

$$= \frac{256.125\angle 128.66^\circ}{9.9\angle 45^\circ}$$

$$= 25.87\angle 83.66^\circ \text{ A}$$

[Comments \(2\)](#)



Anonymous

i think there might be an arithmetic error in this step. i got $(7-j9)\mathbf{I} + 160 - j200 = 0$



Anonymous

Λ nevermind it should be $+j8$ in the first line

Step 3 of 8

Apply Kirchhoff's voltage law around left loop.

$$-200\angle 90^\circ + 5\mathbf{I} - j6\mathbf{I} - j2\mathbf{I} + \mathbf{V}_{Th} = 0$$

$$-200\angle 90^\circ + \mathbf{I}(5 + j4) + \mathbf{V}_{Th} = 0$$

Substitute $25.87\angle 83.66^\circ \text{ A}$ for $\mathbf{I}$.

$$-200\angle 90^\circ + (25.87\angle 83.66^\circ \text{ A})(6.40\angle 38.65^\circ) + \mathbf{V}_{Th} = 0$$

$$-200\angle 90^\circ + 165.66\angle 122.31^\circ + \mathbf{V}_{Th} = 0$$

$$-j200 - 88.57 + j140 + \mathbf{V}_{Th} = 0$$

$$\mathbf{V}_{Th} = 88.57 + j60 \text{ V}$$

$$= 107\angle 34.11^\circ \text{ V}$$

Thus, the Thevenin's voltage $\mathbf{V}_{Th}$ is $107\angle 34.11^\circ \text{ V}$.

Step 4 of 8

To obtain $\mathbf{Z}_{th}$ insert 1A current source as test source and replace all the voltage sources with short circuit.

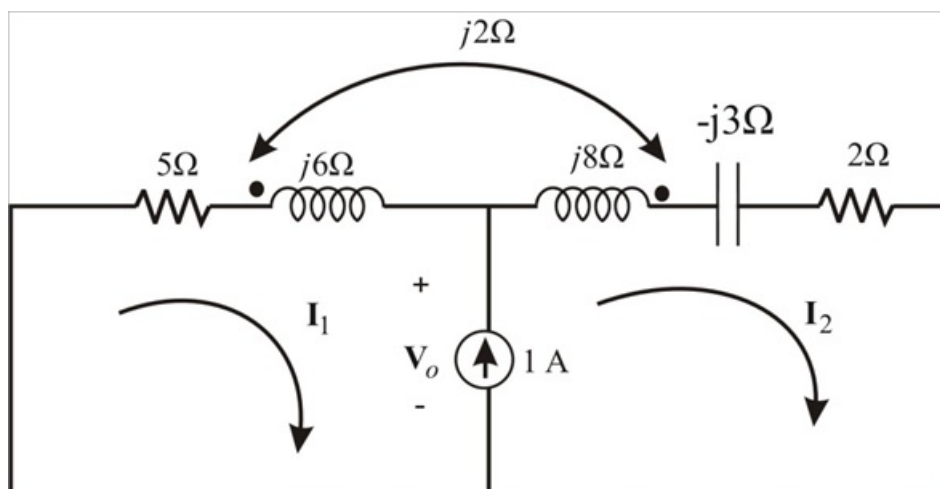


Figure 2

Step 5 of 8

Write the super mesh equation.

$$\mathbf{I}_2 - \mathbf{I}_1 = 0$$

$$\mathbf{I}_2 = \mathbf{I}_1 + 1$$

Apply Kirchhoff's voltage law around outer loop.

$$(5 + j6)\mathbf{I}_1 - j2\mathbf{I}_2 + j8\mathbf{I}_2 - j2\mathbf{I}_1 + (2 - j3)\mathbf{I}_2 = 0$$

$$\mathbf{I}_1(5 + j4) + \mathbf{I}_2(2 + j3) = 0$$

Substitute $\mathbf{I}_1 + 1$ for $\mathbf{I}_2$ in the equation.

$$\mathbf{I}_1(5 + j4) + (\mathbf{I}_1 + 1)(2 + j3) = 0$$

$$\mathbf{I}_1(5 + j4 + 2 + j3) + 2 + j3 = 0$$

$$\mathbf{I}_1(7 + j7) = -(2 + j3)$$

$$\mathbf{I}_1 = 0.3642 \angle -168.69^\circ \text{ A}$$

[Comments \(2\)](#)



Anonymous

Shouldn't the first constraint equation be $\mathbf{I}_2 - \mathbf{I}_1 = 1\text{A}??$



Anonymous

^You're right

Step 6 of 8

Apply Kirchhoff's voltage around left side loop.

$$\mathbf{V}_o + (5 + j6)\mathbf{I}_1 - j2\mathbf{I}_2 = 0$$

$$\mathbf{V}_o + (5 + j6)\mathbf{I}_1 - j2(\mathbf{I}_1 + 1) = 0$$

$$\mathbf{V}_o + (5 + j4)\mathbf{I}_1 - j2 = 0$$

$$\mathbf{V}_o - \frac{(2 + j3)(5 + j4)}{7 + j7} - j2 = 0$$

$$\mathbf{V}_o = 1.5 + j3.786 \Omega$$

Step 7 of 8

Thevenin's impedance is

$$\begin{aligned} \mathbf{Z}_{th} &= \frac{\mathbf{V}_o}{1 \text{ A}} \\ &= \frac{1.5 + j3.786}{1 \text{ A}} \end{aligned}$$

Therefore, the Thevenin's impedance $\mathbf{Z}_{th}$ is $1.5 + j3.786 \Omega$.

[Comments \(1\)](#)



Anonymous

Since, there's no dependent sources, can't you just find $\mathbf{Z}_{th}$ by the sum of the left parallel to the sum of the right??

Step 8 of 8

The Thevenin's equivalent circuit is shown in Figure 3.

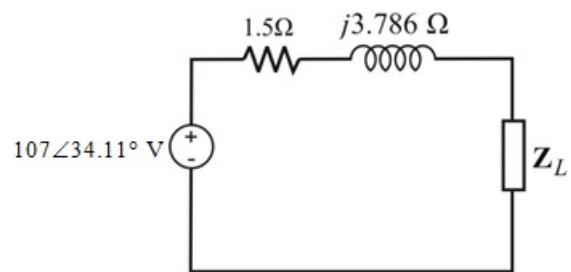


Figure 3

Therefore, the Thevenin's equivalent circuit is shown in Figure 3.