

Problem

Calculate the turns ratio of an ideal transformer required to match a $8\text{-}\Omega$ load to a source with internal impedance of $800\text{ }\Omega$. Find the load voltage when the source voltage is 300 V .

Step-by-step solution

Step 1 of 3

From the transformation ratio of a transformer,

$$V_1 = \frac{V_2}{n}$$

$$I_1 = nI_2$$

The input impedance as seen from the source is,

$$\begin{aligned} Z_{\text{in}} &= \frac{V_1}{I_1} \\ &= \frac{1}{n^2} \frac{V_2}{I_2} \\ &= \frac{Z_L}{n^2} \end{aligned}$$

$$\text{where } Z_L = \frac{V_2}{I_2}$$

Step 2 of 3

Calculate the value of turns ratio.

$$\begin{aligned} n^2 &= \frac{Z_L}{Z_{\text{in}}} \\ n &= \sqrt{\frac{Z_L}{Z_{\text{in}}}} \end{aligned}$$

Substitute $8\text{ }\Omega$ for Z_L and $800\text{ }\Omega$ for Z_{in} .

$$\begin{aligned} n &= \sqrt{\frac{8}{800}} \\ &= \sqrt{\frac{1}{100}} \\ &= 0.1 \end{aligned}$$

Thus, the value of turns ratio is 0.1.

Step 3 of 3

Calculate the value of load voltage, V_L .

$$\frac{V_L}{V_s} = n$$

$$V_L = nV_s$$

Substitute 0.1 for n and 300 V for V_s .

$$\begin{aligned} V_L &= 0.1 \times 300 \\ &= 30 \text{ V} \end{aligned}$$

Thus, the value of the load voltage is 30 V .