

Problem


In the circuit of Fig. 13.93,

(a) find the coupling coefficient,

(b) calculate v_o ,

(c) determine the energy stored in the coupled inductors at $t = 2$ s.

Figure 13.93

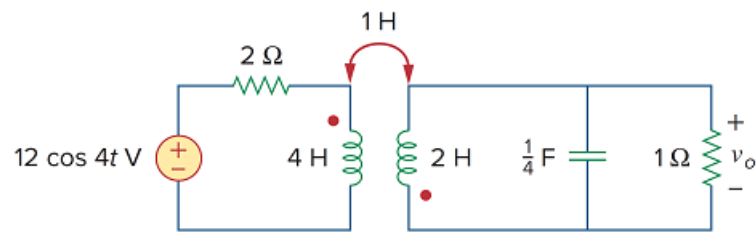

Step-by-step solution

Step 1 of 11

(a)

Refer to circuit diagram in Figure 13.93 in the text book.

Determine the value of coupling coefficient.

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

Substitute 4 H for L_1 , 2 H for L_2 and 1 H for M .

$$\begin{aligned} k &= \frac{1}{\sqrt{(4)(2)}} \\ &= \frac{1}{\sqrt{8}} \\ &= 0.3535 \end{aligned}$$

Therefore, the value of coupling coefficient k is 0.3535.

Step 2 of 11

(b)

The value of frequency is,

$$\omega = 4 \text{ rad/s}$$

Calculate the impedance value of the 4 H inductor.

$$\begin{aligned} j\omega L_1 &= j(4)(4) \\ &= j16 \, \Omega \end{aligned}$$

Calculate the impedance value of the 2 H inductor.

$$\begin{aligned} j\omega L_2 &= j(4)(2) \\ &= j8 \, \Omega \end{aligned}$$

Calculate the impedance value of the 1 H mutual inductor.

$$\begin{aligned} j\omega M &= j(4)(1) \\ &= j4 \, \Omega \end{aligned}$$

Calculate the impedance value of the capacitor.

$$\begin{aligned} \frac{1}{j\omega C} &= \frac{1}{j(4)\left(\frac{1}{4}\right)} \\ &= -j \, \Omega \end{aligned}$$

Step 3 of 11

The frequency domain circuit is shown in Figure 1.

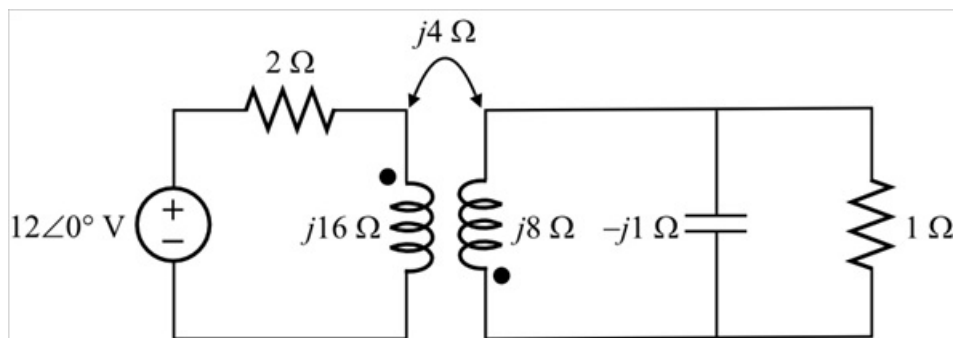


Figure 1

Step 4 of 11

In the circuit, capacitor and $1 \, \Omega$ resistor are connected in parallel. Calculate the equivalent impedance.

$$\begin{aligned} Z_{\text{eq}} &= (1 \, \Omega) \parallel (-j \, \Omega) \\ &= \frac{(1 \, \Omega)(-j \, \Omega)}{1 - j \, \Omega} \\ &= \frac{-j \, \Omega}{1 - j} \\ &= 0.5(1 - j) \, \Omega \end{aligned}$$

Step 5 of 11

The reduced frequency domain circuit is shown in Figure 2.

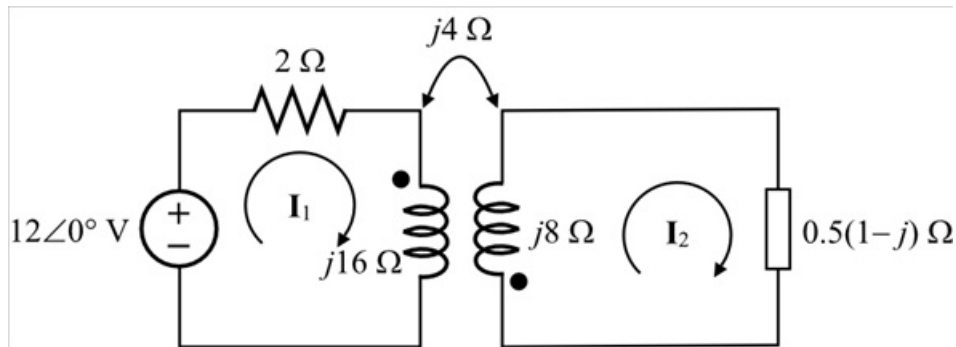


Figure 2

Step 6 of 11

Apply Kirchhoff's voltage law to first loop.

$$-12\angle 0^\circ + 2(I_1) + (j16)(I_1) + (j4)(I_2) = 0$$

$$(2 + j16)(I_1) + (j4)(I_2) = 12$$

$$(1 + j8)I_1 + (j2)I_2 = 6 \dots\dots (1)$$

Apply Kirchhoff's voltage law to second loop.

$$(j4)I_1 + (0.5 - j0.5)I_2 + (j8)I_2 = 0$$

$$(j4)I_1 + (0.5 + j7.5)I_2 = 0$$

$$(j4)I_1 = -(0.5 + j7.5)I_2$$

$$I_1 = -\left(\frac{0.5 + j7.5}{j4}\right)I_2 \dots\dots (2)$$

Step 7 of 11

Recall equation (1).

$$(1 + j8)I_1 + (j2)I_2 = 6$$

Substitute $-\left(\frac{0.5 + j7.5}{j4}\right)I_2$ for I_1 .

$$-(1 + j8)\left(\frac{0.5 + j7.5}{j4}\right)I_2 + (j2)I_2 = 6$$

$$-(2.875 + j14.875)I_2 + (j2)I_2 = 6$$

$$-(2.875 + j12.875)I_2 = 6$$

$$I_2 = \frac{-6}{2.875 + j12.875}$$

$$= -0.099 + j0.4438 \text{ A}$$

Step 8 of 11

Determine the value of output voltage.

$$\mathbf{V}_o = 0.5(1 - j1)\mathbf{I}_2$$

Substitute $-0.099 + j0.4438$ A for $\mathbf{I}_2$.

$$\begin{aligned}\mathbf{V}_o &= 0.5(1 - j1)(-0.099 + j0.4438) \\ &= 0.1724 + j0.2715 \\ &= 321.6 \angle -57.58^\circ \text{ mV}\end{aligned}$$

The output voltage in time domain format is,

$$v_o(t) = 321.6 \cos(4t - 57.58^\circ) \text{ mV}$$

Therefore, the output voltage $v_o(t)$ is $\boxed{321.6 \cos(4t - 57.58^\circ) \text{ mV}}$.

Step 9 of 11

(c)

Determine the value of current $\mathbf{I}_1$.

$$\mathbf{I}_1 = -\left(\frac{0.5 + j7.5}{j4}\right)\mathbf{I}_2$$

Substitute $-0.099 + j0.4438$ A for $\mathbf{I}_2$.

$$\begin{aligned}\mathbf{I}_1 &= -\left(\frac{0.5 + j7.5}{j4}\right)(-0.099 + j0.4438) \\ &= -0.13 + j0.8445 \\ &= 0.8545 \angle -81.21^\circ \text{ A}\end{aligned}$$

$$i_1(t) = 0.8545 \cos(4t - 81.21^\circ) \text{ A}$$

Calculate the current $i_1(t)$ at $t = 2$ s.

$$\begin{aligned}i_1(t) &= 0.8545 \cos\left((4)(2) - (81.21^\circ)\left(\frac{\pi}{180^\circ}\right)\right) \text{ A} \\ &= 0.8545 \cos(8 - 1.417) \text{ A} \\ &= (0.8545)(0.9556) \text{ A} \\ &= 0.8165 \text{ A}\end{aligned}$$

Step 10 of 11

The current $\mathbf{I}_2$ is,

$$\begin{aligned}\mathbf{I}_2 &= -0.099 + j0.4438 \text{ A} \\ &= 0.4547 \cos(4t + 102.59^\circ) \text{ A}\end{aligned}$$

$$i_2(t) = 0.4547 \cos(4t + 102.59^\circ) \text{ A}$$

Calculate the current $i_2(t)$ at $t = 2$ s.

$$\begin{aligned}i_2(t) &= 0.4547 \cos\left((4)(2) + (102.59^\circ)\left(\frac{\pi}{180^\circ}\right)\right) \text{ A} \\ &= 0.4547 \cos(8 + 1.79) \text{ A} \\ &= (0.4547)(-0.9338) \text{ A} \\ &= -0.4246 \text{ A}\end{aligned}$$

Step 11 of 11

Determine the energy stored in the coupled inductors at $t = 2 \text{ s}$.

$$\begin{aligned} W &= \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2 \\ &= \frac{1}{2} (4) (0.8165)^2 + \frac{1}{2} (2) (-0.4246)^2 + (1) (0.8165) (-0.4246) \\ &= 1.333 + 0.1803 - 0.3467 \\ &= 1.167 \text{ J} \end{aligned}$$

Therefore, the energy stored in the coupled inductors at $t = 2 \text{ s}$ is 1.167 J.