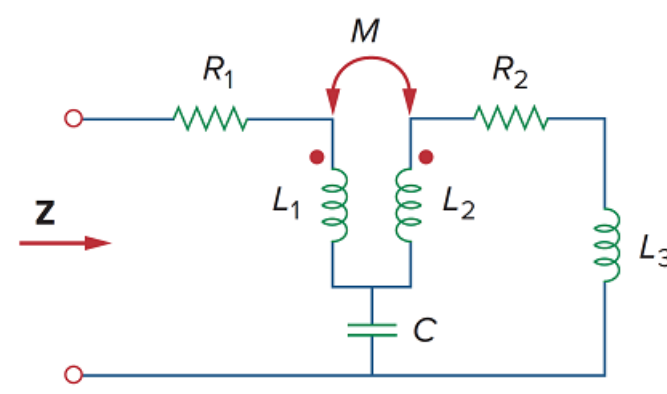


Problem

Using Fig. 13.103, design a problem to help other students better understand how to find the input impedance of circuits with transformers.

Figure 13.103




Step-by-step solution

Step 1 of 4

Refer to circuit diagram in Figure 13.103 in the textbook.

Draw the frequency domain circuit.

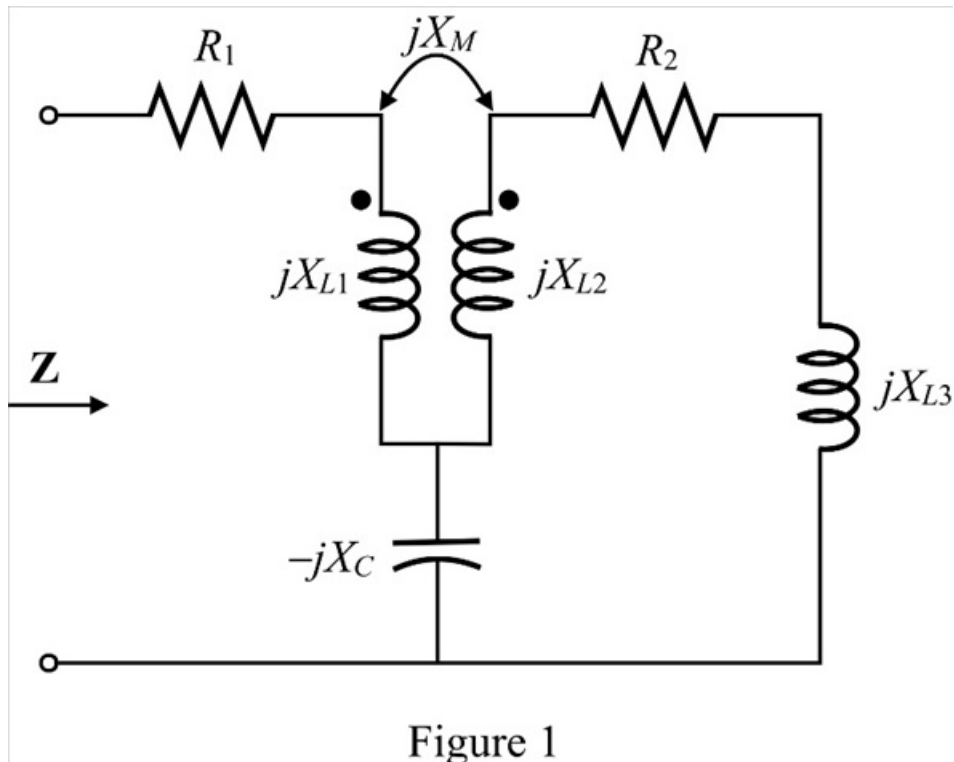

Step 2 of 4

Now, convert linear transformer into an equivalent T circuit. The circuit diagrams of linear transformer and equivalent T network is shown in Figure 2.

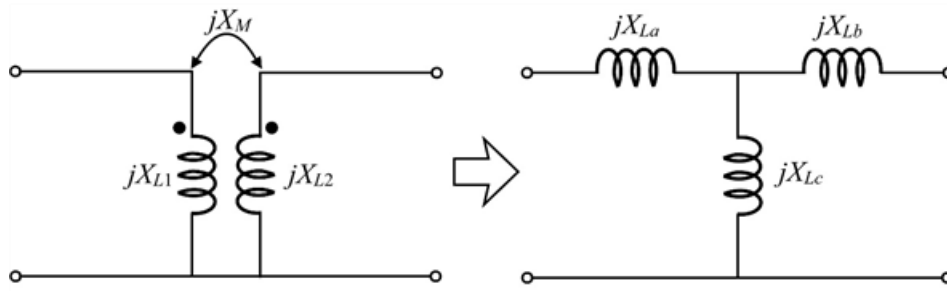


Figure 2

Step 3 of 4

Calculate the value of impedance jX_{La} .

$$jX_{La} = jX_{L1} - jX_M$$

Calculate the value of impedance jX_{Lb} .

$$jX_{Lb} = jX_{L2} - jX_M$$

Calculate the value of impedance jX_{Lc} .

$$jX_{Lc} = jX_M$$

The modified circuit diagram is shown in Figure 3.

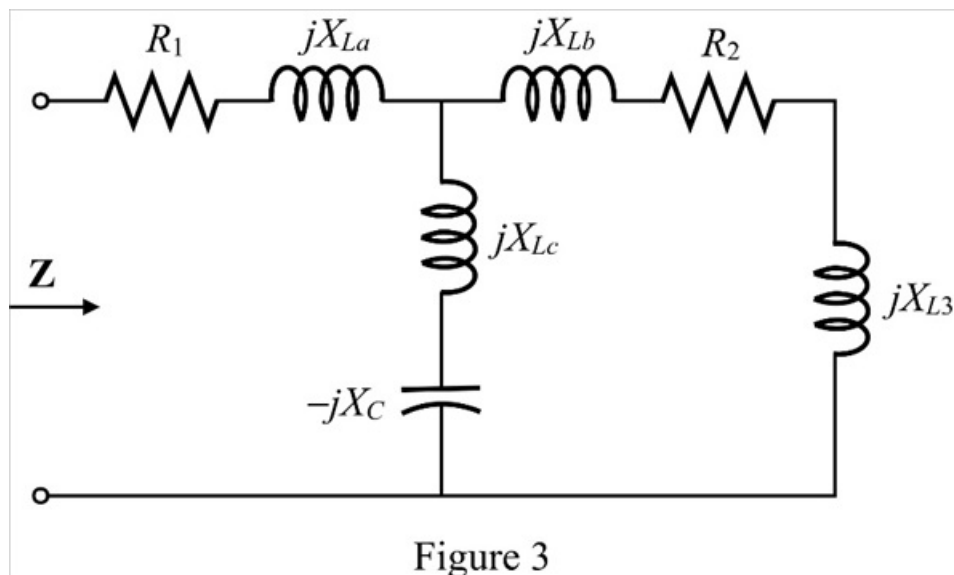


Figure 3

Step 4 of 4

Calculate the input impedance of the circuit.

$$\mathbf{Z} = R_1 + jX_{L1} + (jX_{Lc} - jX_C) \parallel (jX_{L2} + R_2 + jX_{L3})$$

Substitute $jX_{L1} - jX_M$ for jX_{L1} , $jX_{L2} - jX_M$ for jX_{L2} and jX_M for jX_{Lc} .

$$\begin{aligned} \mathbf{Z} &= R_1 + jX_{L1} - jX_M + (jX_M - jX_C) \parallel (jX_{L2} - jX_M + R_2 + jX_{L3}) \\ &= R_1 + jX_{L1} - jX_M + \frac{(jX_M - jX_C)(jX_{L2} - jX_M + R_2 + jX_{L3})}{jX_M - jX_C + jX_{L2} - jX_M + R_2 + jX_{L3}} \\ &= R_1 + jX_{L1} - jX_M + \frac{\begin{pmatrix} -X_{L2}X_M + X_M^2 + jR_2X_M - X_{L3}X_M + \\ X_{L2}X_C - X_MX_C - jR_2X_C + X_{L3}X_C \end{pmatrix}}{-jX_C + jX_{L2} + R_2 + jX_{L3}} \\ &= \frac{(R_1 + jX_{L1} - jX_M) \begin{pmatrix} -jX_C + jX_{L2} + \\ R_2 + jX_{L3} \end{pmatrix} + \begin{pmatrix} -X_{L2}X_M + X_M^2 + jR_2X_M - X_{L3}X_M + \\ X_{L2}X_C - X_MX_C - jR_2X_C + X_{L3}X_C \end{pmatrix}}{-jX_C + jX_{L2} + R_2 + jX_{L3}} \\ &= \frac{\begin{pmatrix} -jR_1X_C + jR_1X_{L2} + R_1R_2 + jR_1X_{L3} + \\ X_{L1}X_C - X_{L1}X_{L2} + jR_2X_{L1} - X_{L1}X_{L3} \\ -X_MX_C + X_MX_{L2} - jR_2X_M + X_MX_{L3} \end{pmatrix} + \begin{pmatrix} -X_{L2}X_M + X_M^2 + jR_2X_M - X_{L3}X_M + \\ X_{L2}X_C - X_MX_C - jR_2X_C + X_{L3}X_C \end{pmatrix}}{-jX_C + jX_{L2} + R_2 + jX_{L3}} \\ &= \frac{\begin{pmatrix} jR_1(X_{L2} + X_{L3} - X_C) + jR_2(X_{L1} - X_C) + R_1R_2 + \\ X_{L1}(X_C - X_{L2} - X_{L3}) + X_M(X_M - 2X_C) + X_C(X_{L2} + X_{L3}) \end{pmatrix}}{-jX_C + jX_{L2} + R_2 + jX_{L3}} \end{aligned}$$

Therefore, the input impedance, $\mathbf{Z}$ of the circuit is,

$$\boxed{\frac{\begin{pmatrix} jR_1(X_{L2} + X_{L3} - X_C) + jR_2(X_{L1} - X_C) + R_1R_2 + \\ X_{L1}(X_C - X_{L2} - X_{L3}) + X_M(X_M - 2X_C) + X_C(X_{L2} + X_{L3}) \end{pmatrix}}{-jX_C + jX_{L2} + R_2 + jX_{L3}}}$$