

Problem

A 1,200/240-V rms transformer has impedance $60 \angle -30^\circ \Omega$ on the high-voltage side. If the transformer is connected to a $0.8 \angle 10^\circ \Omega$ load on the low-voltage side, determine the primary and secondary currents when the transformer is connected to 1,200 V rms.

Step-by-step solution

Step 1 of 4

The primary voltage of the transformer is, $V_1 = 1200 \text{ V}$

The secondary voltage of the transformer is, $V_2 = 240 \text{ V}$

Determine the turns ratio or transformation ratio of the transformer.

$$\begin{aligned} n &= \frac{N_2}{N_1} \\ &= \frac{V_2}{V_1} \\ &= \frac{240}{1200} \\ &= 0.2 \end{aligned}$$

Step 2 of 4

The value of load impedance is, $Z_L = 0.8 \angle 10^\circ \Omega$

Determine the load impedance referred to the primary side.

$$\begin{aligned} Z_R &= \frac{Z_L}{n^2} \\ &= \frac{0.8 \angle 10^\circ}{(0.2)^2} \\ &= \frac{0.8 \angle 10^\circ}{0.04} \\ &= 20 \angle 10^\circ \Omega \end{aligned}$$

Step 3 of 4

The impedance in the primary side is, $\mathbf{Z_p = 60\angle -30^\circ \Omega}$

Determine the input impedance of the transformer.

$$\begin{aligned}\mathbf{Z_{in}} &= \mathbf{Z_p + Z_R} \\ &= \mathbf{60\angle -30^\circ + 20\angle 10^\circ} \\ &= \mathbf{76.41\angle -20.31^\circ \Omega}\end{aligned}$$

Determine the primary current, $\mathbf{I_1}$.

$$\begin{aligned}\mathbf{I_1} &= \frac{\mathbf{V_1}}{\mathbf{Z_{in}}} \\ &= \frac{\mathbf{1200}}{\mathbf{76.41\angle -20.31^\circ}} \\ &= \mathbf{15.7\angle 20.31^\circ A}\end{aligned}$$

Therefore, the value of primary current in the transformer, $\mathbf{I_1}$ is $\boxed{15.7\angle 20.31^\circ A}$.

Step 4 of 4

Determine the secondary current, $\mathbf{I_2}$.

$$\begin{aligned}\mathbf{I_2} &= \frac{\mathbf{I_1}}{\mathbf{n}} \\ &= \frac{\mathbf{15.7\angle 20.31^\circ}}{\mathbf{0.2}} \\ &= \mathbf{78.5\angle 20.31^\circ A}\end{aligned}$$

Therefore, the value of secondary current in the transformer, $\mathbf{I_2}$ is $\boxed{78.5\angle 20.31^\circ A}$.