

Problem

The primary of an ideal transformer with a turns ratio of 5 is connected to a voltage source with Thevenin parameters $v_{Th} = 10 \cos 2000t$ V and $R_{Th} = 100 \Omega$. Determine the average power delivered to a $200\text{-}\Omega$ load connected across the secondary winding.

Step-by-step solution

Step 1 of 6

Consider the primary of an ideal transformer with turns ratio 1 is connected to the voltage source $v_{Th} = 10 \cos 2000t$ V and $R_{Th} = 200 \Omega$ as shown in Figure 1.

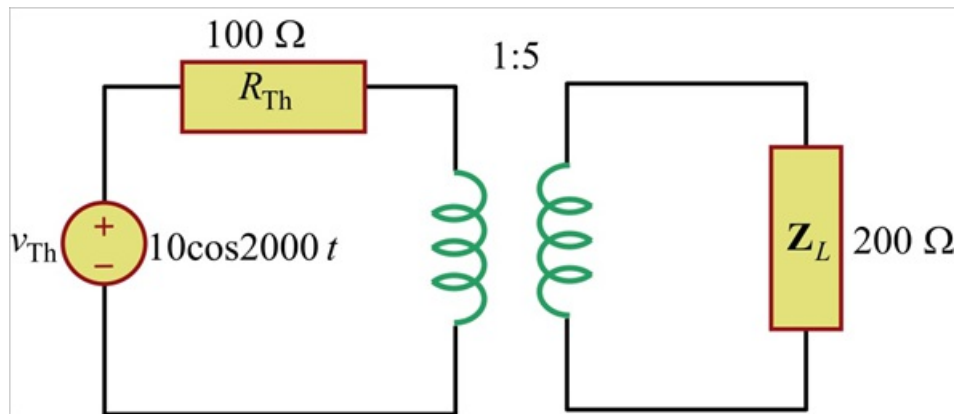


Figure 1

Step 2 of 6

Draw the following circuit diagram the value of Z_{in} input impedance seen at the input side.

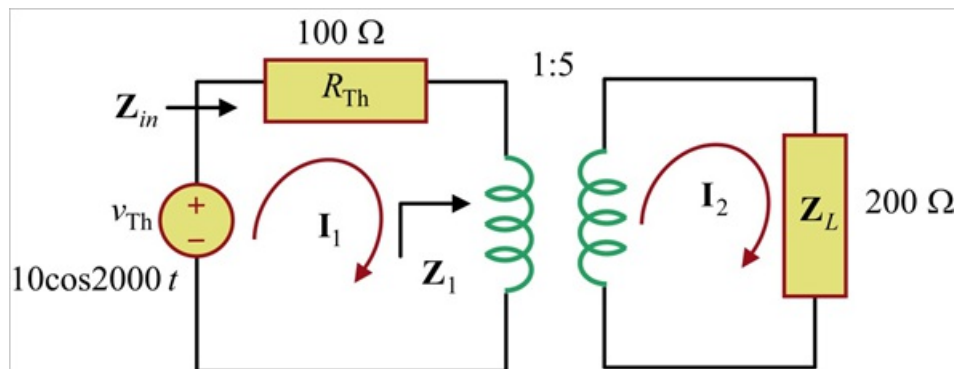


Figure 2

Step 3 of 6

Calculate the value of $\mathbf{Z_1}$.

Write the following expression.

$$\frac{\mathbf{Z_1}}{\mathbf{Z_L}} = \left(\frac{N_1}{N_2} \right)^2$$

$$\mathbf{Z_1} = \left(\frac{N_1}{N_2} \right)^2 \mathbf{Z_L}$$

Substitute 1:5 for $\frac{N_1}{N_2}$, 200 Ω for $\mathbf{Z_L}$ in this expression.

$$\begin{aligned}\mathbf{Z_1} &= \frac{(200)}{(5)^2} \\ &= 8\end{aligned}$$

Therefore, the value of $\mathbf{Z_1}$ is 8 .

Step 4 of 6

Calculate the value of input impedance $\mathbf{Z_{in}}$ seen at the input side.

$$\mathbf{Z_{in}} = \mathbf{Z_p} + \mathbf{Z_1}$$

Substitute 100 Ω for $\mathbf{Z_p}$, 8 for $\mathbf{Z_1}$ in this expression.

$$\begin{aligned}\mathbf{Z_{in}} &= 100 + 8 \Omega \\ &= 108 \Omega\end{aligned}$$

Therefore, the value of $\mathbf{Z_{in}}$ is 108 Ω .

Step 5 of 6

Calculate the value of the current $\mathbf{I_1}$.

Write the expression for the current $\mathbf{I_1}$.

$$\mathbf{I_1} = \frac{\mathbf{V_1}}{\mathbf{Z_{in}}}$$

Substitute 10 V for $\mathbf{V_1}$, 108 Ω for $\mathbf{Z_{in}}$ in this expression.

$$\begin{aligned}\mathbf{I_1} &= \frac{10}{108} \\ &= 92.52 \times 10^{-3}\end{aligned}$$

Therefore, the value of $\mathbf{I_1}$ is 92.52 mA .

Step 6 of 6

Calculate the value of the current $\mathbf{I_2}$.

Write the expression for the current $\mathbf{I_2}$.

$$\frac{\mathbf{I_2}}{\mathbf{I_1}} = \frac{N_1}{N_2}$$
$$\mathbf{I_2} = \left(\frac{N_1}{N_2} \right) \mathbf{I_1}$$

Substitute 1:5 for $\frac{N_1}{N_2}$, 92.52 mA for $\mathbf{I_1}$ in this expression.

$$\mathbf{I_2} = \left(\frac{1}{5} \right) 92.52 \text{ mA}$$
$$= 18.504 \text{ mA}$$

Therefore, the value of $\mathbf{I_2}$ is 18.504 mA .

Calculate the value of P_{avg} average power transferred to the load $\mathbf{Z_L}$.

Write the expression for the value of P_{avg} average power transferred to the load $\mathbf{Z_L}$.

$$P_{avg} = \frac{1}{2} |\mathbf{I_2}|^2 \mathbf{Z_L}$$
$$P_{avg} = \frac{1}{2} |18.504 \text{ mA}|^2 (200)$$
$$= 100 (342.39 \times 10^{-6})$$
$$= 34.3 \times 10^{-3}$$

Therefore, the value of P_{avg} is 34.3 mW .