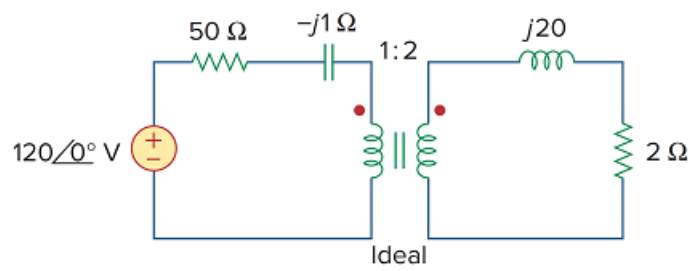


Problem

For the circuit in Fig. 13.107, determine the power absorbed by the $2\text{-}\Omega$ resistor. Assume the 120 V is an rms value.

Figure 13.107



Step-by-step solution

Step 1 of 6

Refer to Figure 13.107 in the textbook for the actual circuit.

Redraw the circuit as follows.

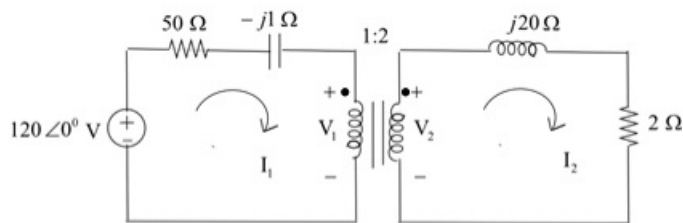


Figure 1

Step 2 of 6

Apply Kirchhoff's voltage law to mesh 1.

$$(50 - j1)I_1 + V_1 - 120 = 0$$

$$(50 - j1)I_1 + V_1 = 120 \quad \text{..... (1)}$$

Apply Kirchhoff's voltage law to mesh 2.

$$(2 + j20)I_2 - V_2 = 0 \quad \text{..... (2)}$$

Step 3 of 6

At the transformer terminals,

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

Substitute 2 for N_2 , 1 for N_1 .

$$\frac{V_2}{V_1} = \frac{2}{1}$$

$$V_1 = \frac{V_2}{2}$$

The primary and secondary currents are related to the turns ratio in the inverse manner.

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

Substitute 2 for N_2 , 1 for N_1 .

$$\frac{I_1}{I_2} = \frac{2}{1}$$

$$I_1 = 2I_2$$

Step 4 of 6

Substitute $\frac{V_2}{2}$ for V_1 and $2I_2$ for I_1 in equation (1).

$$(50 - j1)2I_2 + \frac{V_2}{2} = 120 \quad \dots\dots (3)$$

Multiply equation (3) by 2,

$$(200 - j4)I_2 + V_2 = 240 \quad \dots\dots (4)$$

Step 5 of 6

Add equations (2) and (4).

$$(2 + j20)I_2 - V_2 + (200 - j4)I_2 + V_2 = 240$$

$$(202 + j16)I_2 = 240$$

$$I_2 = \frac{240}{202 + j16}$$

$$I_2 = 1.184 \angle -4.53^\circ \text{ A}$$

Step 6 of 6

Calculate the power absorbed by the 2Ω resistor.

$$P = |I_2|^2 R$$

Substitute 1.184 A for $|I_2|$, 2Ω for R .

$$P = (1.184)^2 (2)$$

$$= (1.4028)(2)$$

$$= 2.805 \text{ W}$$

Therefore, the power absorbed by the 2Ω resistor is 2.805 W .