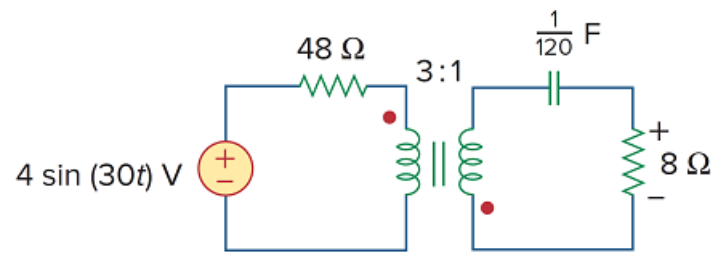


Problem

For the circuit shown in Fig. 13.110, find the value of the average power absorbed by the 8- Ω resistor.

Figure 13.110



Step-by-step solution

Step 1 of 6

Refer to Figure 13.110 in the textbook.

Write the expression for source voltage.

$$\begin{aligned} v_s(t) &= 4 \sin(30t) \\ &= 4 \cos(30t - 90^\circ) \text{ V} \end{aligned}$$

The phasor value of source voltage is,

$$\begin{aligned} \mathbf{V}_s &= 4 \angle -90^\circ \text{ V} \\ \omega &= 30 \text{ rad/s} \end{aligned}$$

Calculate the impedance across the capacitor.

$$\begin{aligned} \mathbf{Z}_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j(30)\left(\frac{1}{120}\right)} \\ &= -j4 \Omega \end{aligned}$$

Step 2 of 6

Draw the circuit in phasor domain.

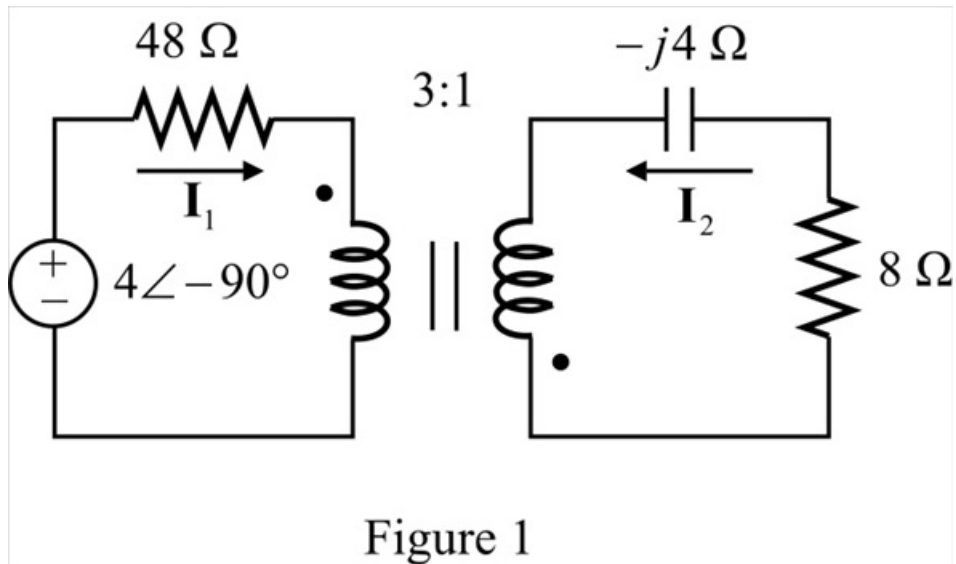


Figure 1

Step 3 of 6

The load impedance across the secondary side is,

$$\mathbf{Z}_L = 8 - j4 \, \Omega$$

Calculate the value of transformer ratio.

$$\begin{aligned} n &= \frac{N_2}{N_1} \\ &= \frac{1}{3} \end{aligned}$$

Move the secondary load impedance to primary.

$$\begin{aligned} \mathbf{Z}_R &= \frac{\mathbf{Z}_L}{n^2} \\ &= \frac{8 - j4}{\left(\frac{1}{3}\right)^2} \\ &= 72 - j36 \, \Omega \end{aligned}$$

Step 4 of 6

Draw the modified circuit diagram.

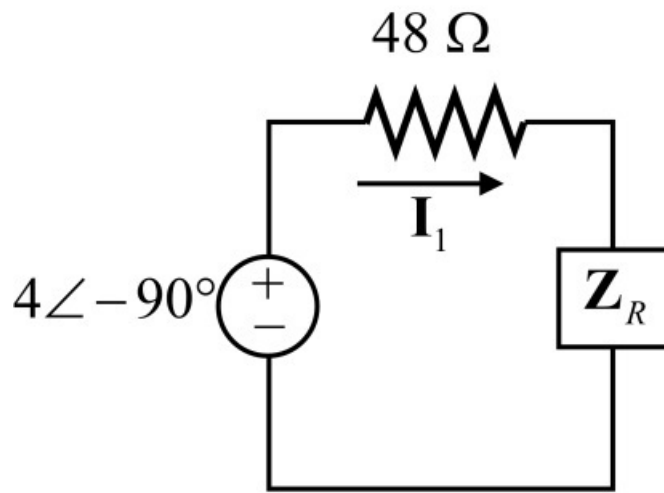


Figure 2

Step 5 of 6

Calculate the value of primary current, I_1 .

$$\begin{aligned} I_1 &= \frac{4\angle -90^\circ}{48 + 72 - j36} \\ &= 31.927\angle -73.3^\circ \text{ mA} \end{aligned}$$

Calculate the value of secondary current, I_2 .

$$\begin{aligned} I_2 &= \frac{N_1}{N_2} \times I_1 \\ &= \frac{3}{1} \times (31.927\angle -73.3^\circ \text{ mA}) \\ &= 95.78\angle -73.3^\circ \text{ mA} \end{aligned}$$

Step 6 of 6

Calculate the power absorbed by the $8\ \Omega$ resistor.

$$\begin{aligned} P_{8\ \Omega} &= \frac{|I_2|^2 R}{2} \\ &= \frac{(95.78 \times 10^{-3})^2 (8)}{2} \\ &= 36.7 \times 10^{-3} \\ &= 36.7 \text{ mW} \end{aligned}$$

Thus, the power absorbed by the $8\ \Omega$ resistor is 36.7 mW.